

A spring with a mass of 2 kg has damping constant 14 kg/s. A force of 3.6 N is required to keep the spring stretched 0.3 m beyond its natural length. The spring is stretched 0.8 m beyond natural length and released. If an external force of $F_e(t) = 10e^{-t}$ N is applied to the spring, find the position at time t .

$$mx'' + cx' + kx = F_e$$

$$F = kx$$

$$2x'' + 14x' + 12x = 10e^{-t}$$

$$k = \frac{F}{x}$$

Auxiliary Equation

$$= 12$$

$$2r^2 + 14r + 12 = 0$$

$$r^2 + 7r + 6 = 0$$

$$(r+1)(r+6) = 0$$

$$r = -1 \quad r = -6$$

Complementary Equation

$$x_c(t) = C_1 e^{-x} + C_2 e^{-6x}$$

Assume $x_p(t)$ is exponential

$$x_p(t) = Ae^{-t}$$

$$x_p'(t) = -Ae^{-t}$$

$$x_p''(t) = Ae^{-t}$$

Sub and solve

$$2(Ae^{-t}) + 14(-Ae^{-t}) + 12(Ae^{-t}) = 10e^{-t}$$

$$0 = 10$$

Multiply by t

$$x_p(t) = Ate^{-t}$$

$$x_p'(t) = A(t \cdot -e^{-t} + e^{-t})$$

$$= A(-te^{-t} + e^{-t})$$

$$= -Ate^{-t} + Ae^{-t}$$

$$x_p''(t) = -A(t \cdot -e^{-t} + e^{-t}) - Ae^{-t}$$

$$= -A(-te^{-t} + e^{-t}) - Ae^{-t}$$

$$= Ate^{-t} - Ae^{-t} - Ae^{-t}$$

$$= Ate^{-t} - 2Ae^{-t}$$

Sub and solve

$$2(Ate^{-t} - 2Ae^{-t}) + 4(-Ate^{-t} + Ae^{-t}) + 12(Ate^{-t}) = 10e^{-t}$$

$$2Ate^{-t} - 4Ae^{-t} - 4Ate^{-t} + 4Ae^{-t} + 12Ate^{-t} = 10e^{-t}$$

$$2At - 4A - 4At + 4A + 12At = 10$$

$$10A = 10$$

$$A = 1$$

$$x_p(t) = te^{-t}$$

General Solution

$$x(t) = C_1 e^{-t} + C_2 e^{-6t} + te^{-t}$$

$$x'(t) = -C_1 e^{-t} - 6C_2 e^{-6t} + t \cdot -e^{-t} + e^{-t}$$

$$= -C_1 e^{-t} - 6C_2 e^{-6t} - te^{-t} + e^{-t}$$

Initial Condition $x(0) = 0.8 \text{ m}$ and $x'(0) = 0$

$$0.8 = C_1 e^0 + C_2 e^0 + 0$$

$$0 = -C_1 e^0 - 6C_2 e^0 - 0 + 1$$

$$0.8 = C_1 + C_2$$

$$0 = -C_1 - 6C_2 + 1$$

$$0.8 = -5C_2 + 1$$

$$-0.2 = -5C_2$$

$$C_2 = 0.04$$

$$C_1 = 0.76$$

Unique Solution

$$x(t) = 0.76e^{-t} + 0.04te^{-6t} + te^{-t}$$

A spring with a mass of 1 kg has a spring constant 43 kg/s². If the spring begins at equilibrium position and is given a velocity of 3 m/s, find the damping constant that would produce critical damping.

$$m \frac{d^2x}{dt^2} + c \frac{dx}{dt} + kx = 0$$

$$\text{Critical Damping: } c^2 - 4mk = 0$$

$$c^2 = 4mk$$

$$c = \sqrt{4mk}$$

$$= 2\sqrt{43}$$

A spring with a 4 kg mass will stretch 0.5 m past rest with a force of 12 N. The spring starts at equilibrium and is pushed to the right with an initial value of 3 m/s. Find position at time t .

$$m \frac{d^2x}{dt^2} + c \frac{dx}{dt} + kx = 0$$

$$k = \frac{F}{x}$$

$$4x'' + 0 + 24x = 0$$

$$= 24$$

Auxiliary Equation

$$4r^2 + 24 = 0$$

$$r^2 + 6 = 0$$

$$r^2 = -6$$

$$r = 0 \pm \sqrt{6}i; \quad \alpha = 0 \quad \beta = \sqrt{6}$$

General Solution

$$x(t) = e^0 (C_1 \sin(\sqrt{6}t) + C_2 \cos(\sqrt{6}t))$$

$$= C_1 \sin(\sqrt{6}t) + C_2 \cos(\sqrt{6}t)$$

$$x'(t) = \sqrt{6}C_1 \cos(\sqrt{6}t) - \sqrt{6}C_2 \sin(\sqrt{6}t)$$

Initial Values $x(0) = 0\text{m}$ and $x'(0) = 3\text{m/s}$

$$0 = C_1 \sin(0) + C_2 \cos(0)$$

$$3 = \sqrt{6} C_1 \cos(0) - \sqrt{6} C_2 \sin(0)$$

$$0 = C_2$$

$$3 = \sqrt{6} C_1$$

$$C_2 = 0$$

$$C_1 = \frac{3}{\sqrt{6}}$$

Unique Solution

$$x(t) = \frac{3}{\sqrt{6}} \sin(\sqrt{6} t)$$

A series circuit consists of a resistor with $R = 20\Omega$, an inductor with $L = 1\text{H}$, a capacitor with $C = 0.01\text{F}$, and a 9V battery. Its initial charge and current are initially 0 . Find charge and current as a function of time.

$$L \frac{d^2 Q}{dt^2} + R \frac{dQ}{dt} + \frac{1}{C} Q = 19$$

$$1Q'' + 20Q' + 100Q = 19$$

Auxiliary Equation

$$r^2 + 20r + 100 = 0$$

$$r = \frac{-20 \pm \sqrt{400 - 400}}{2}$$

$$= -10$$

Complementary Solution

$$Q_c(t) = C_1 e^{10t} + C_2 t e^{10t}$$

Assume the particular solution is a constant

$$Q_p(t) = A$$

$$Q_p'(t) = 0$$

$$Q_p''(t) = 0$$

Sub and solve

$$0 + 0 + A \cdot 100 = 19$$

$$A = \frac{19}{100}$$

$$Q_p(t) = \frac{19}{100}$$

General Solution

$$Q(x) = C_1 e^{-10t} + C_2 t e^{-10t} + \frac{19}{100}$$

$$I(x) = -10C_1 e^{-10t} + C_2(-10te^{-10t} + e^{-10t})$$

$$= -10C_1 e^{-10t} - 10C_2 t e^{-10t} + C_2 e^{-10t}$$

Initial Condition $Q(0) = 0$ and $I(0) = 0$

$$0 = C_1 e^0 + \frac{19}{100}$$

$$0 = -10C_1 e^0 + C_2 e^0$$

$$0 = C_1 + \frac{19}{100}$$

$$0 = -10C_1 + C_2$$

$$C_1 = -\frac{19}{100}$$

$$0 = -10\left(-\frac{19}{100}\right) + C_2$$

$$0 = \frac{190}{100} + C_2$$

$$C_2 = -\frac{19}{10}$$

Unique Solution

$$= -10C_1 e^{-10t} - 10C_2 t e^{-10t} + C_2 e^{-10t}$$

$$Q(t) = -\frac{19}{100} e^{-10t} - \frac{19}{10} t e^{-10t} + \frac{19}{100}$$

$$I(t) = -10\left(-\frac{19}{100}\right) e^{-10t} - 10\left(-\frac{19}{10}\right) t e^{-10t} + \left(-\frac{19}{10}\right) e^{-10t}$$

$$= \frac{19}{10} e^{-10t} + 19 t e^{-10t} - \frac{19}{10} e^{-10t}$$

A series circuit consists of a resistor with $R=20\Omega$, an inductor with $L=1H$, a capacitor with $C=0.01F$, and a generator producing a voltage of $E(t)=160\sin(10t)$. Initial charge and current are 0. Find charge and current at time t .

Let the general solution of the problem above be the complementary solution

$$Q_c(x) = C_1 e^{-10t} + C_2 t e^{-10t}$$

Assume the particular solution is trigonometric.

$$Q_p(x) = A\sin(10t) + B\cos(10t)$$

$$Q_p'(x) = 10A\cos(10t) - 10B\sin(10t)$$

$$Q''_p(x) = -100A\sin(10t) - 100B\cos(10t)$$

Sub and solve

$$(-100A\sin(10t) - 100B\cos(10t)) + 20(10A\cos(10t) - 10B\sin(10t)) + 100(A\sin(10t) + B\cos(10t)) = 160\sin(10t)$$

~~$$-100A\sin(10t) - 100B\cos(10t) + 200A\cos(10t) - 200B\sin(10t) + 100A\sin(10t) + 100B\cos(10t) = 160\sin(10t)$$~~

$$\rightarrow -200B \sin(10t) = 160 \sin(10t)$$

$$200A \cos(10t) = 0$$

$$-200B = 160$$

$$A = 0$$

$$B = -\frac{160}{200}$$

$$= -\frac{4}{5}$$

$$Q_p(x) = -\frac{4}{5} \cos(10t)$$

General Solution

$$Q(x) = C_1 e^{-10t} + C_2 t e^{-10t} - \frac{4}{5} \cos(10t)$$

$$Q''(x) = -10C_1 e^{-10t} + C_2(-10t e^{-10t} + e^{-10t}) + 8 \sin(10t)$$

$$= -10C_1 e^{-10t} - 10C_2 t e^{-10t} + C_2 e^{-10t} + 8 \sin(10t)$$

Initial Values $Q(0) = 0$ and $Q'(0) = 0$

$$0 = C_1 e^0 + 0 - \frac{4}{5} \cos(0)$$

$$0 = -10C_1 e^0 - 0 + C_2 e^0 - 8 \sin(0)$$

$$0 = C_1 - \frac{4}{5}$$

$$0 = -10C_1 + C_2$$

$$C_1 = \frac{4}{5}$$

$$0 = -10\left(\frac{4}{5}\right) + C_2$$

$$0 = -\frac{40}{5} + C_2$$

$$C_2 = \frac{40}{5}$$

$$= 8$$

Unique Solution

$$Q(x) = \frac{4}{5}e^{-10t} + 8te^{-10t} - \frac{4}{5}\cos(10t)$$

$$I(x) = -10\left(\frac{4}{5}\right)e^{-10t} - 10(8)te^{-10t} + (8)e^{-10t} + \frac{4}{5}\sin(10t)$$

$$= -8e^{-10t} - 80te^{-10t} + 8e^{-10t} + 8\sin(10t)$$

A series circuit consists of a resistor with $R = 20 \Omega$, a capacitor with $C = 0.01 \text{ F}$, and a decaying battery with $E(t) = 500e^{-5t}$. If the initial charge is 0, find charge as a function of time.

$$LQ'' + RQ' + \frac{1}{C}Q = E(t)$$

$$20Q' + 100Q = 500e^{-5t}$$

$$Q' + 5Q = 25e^{-5t}$$

Auxiliary Equation

$$r + s = 0$$

$$r = -s$$

Complementary Solution

$$Q_c(t) = C_1 e^{-st}$$

Assume the particular solution is exponential

$$Q_p(t) = A e^{-st}$$

$$Q_p'(t) = -s A e^{-st}$$

Sub and solve

$$(-s A e^{-st}) + s(A e^{-st}) = s C_0 e^{-st}$$

$$C = s C_0$$

Multiply by x

$$Q_p(t) = A t e^{-st}$$

$$Q_p'(t) = A(t \cdot -s e^{-st} + e^{-st})$$

$$= -SAte^{-st} + Ae^{-st}$$

Sub and solve

$$(-SAte^{-st} + Ae^{-st}) + S(Ate^{-st}) = 2Se^{-st}$$

$$Ae^{-st} = 2Se^{-st}$$

$$A = 2S$$

$$Q_p(t) = 2Ste^{-st}$$

General Solution

$$Q(t) = C_1 e^{-st} + 2Ste^{-st}$$

Initial Value $Q(0) = 0$

$$0 = C_1 e^0 + 0$$

$$C_1 = 0$$

Unique Solution

$$Q(t) = 2Ste^{-st}$$