


Homework 2

To receive full credits, you must describe the reasoning behind each step, e.g. KVL on $L1$, or using Ohm's law on $R1$, etc. Problems without reasoning receive 0 points regardless of providing correct or incorrect result. Problems with clear reasoning and correct result receives full points. Solutions with clear reasoning and incorrect results receive 3/4 of the total points.

Use the branch current method to solve the following problems.


Problem 1: Solve for V_x . (10 points)

$V_{s1} = 2\text{ V}$ $V_{s2} = 1\text{ V}$ $V_{s3} = 6\text{ V}$
 $R_1 = 1\ \Omega$ $R_2 = 3\ \Omega$ $R_3 = 10\ \Omega$

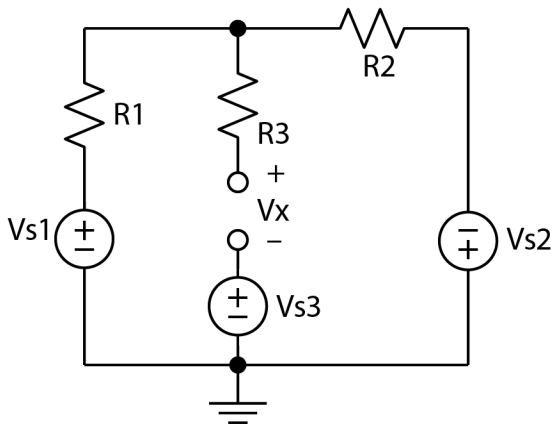

Problem 2: Solve for V_x . (10 points)

$I_{s1} = 1\text{ A}$ $I_{s2} = 2\text{ A}$
 $R_1 = 10\ \Omega$ $R_2 = 2\ \Omega$ $R_3 = 6\ \Omega$ $R_4 = 5\ \Omega$

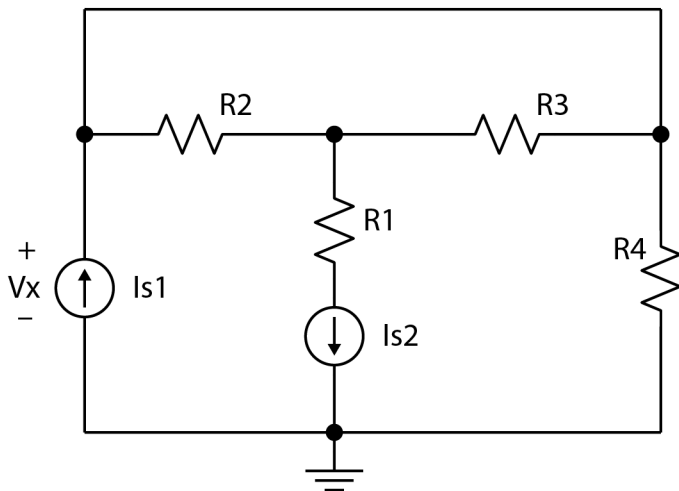


Problem 3: The following circuit has a switch S1.

- Solve for V_x when the switch S1 is open. (10 points)
- Solve for V_x when the switch S1 is closed. (10 points)

$$I_{s1} = 5 \text{ A} \quad V_{s1} = 5 \text{ V}$$

$$R_1 = 20 \, \Omega \quad R_2 = 50 \, \Omega \quad R_3 = 100 \, \Omega \quad R_x = 30 \, \Omega$$

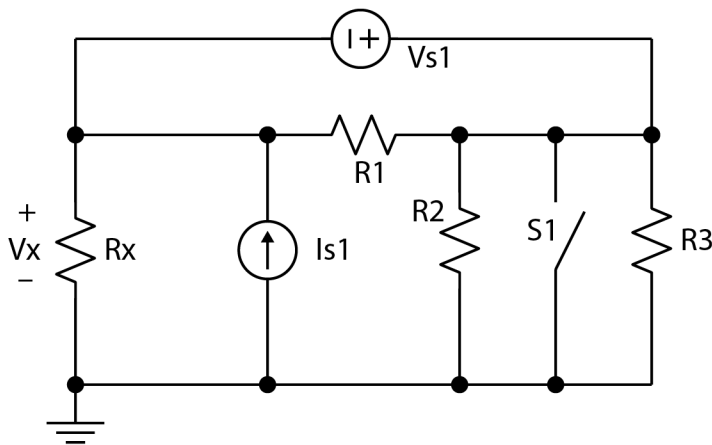


Problem 4: The circuit below contains a potentiometer whose programmable resistance is R .

- Solve for I_x and express the result as a function of R and V_{s2} . (20 points)

$$V_{s1} = 10 \text{ V} \quad I_{s1} = 1 \text{ A}$$


$$R_1 = 5 \, \Omega \quad R_2 = 50 \, \Omega$$

- Find the value of the potentiometer R such that $I_x = 0.5 I_{s1}$. Use $V_{s2} = 10 \text{ V}$. (5 points)
- For the potentiometer value found in "b)", find the value for the V_{s2} such that $I_x = -0.5 I_{s1}$. (5 points)

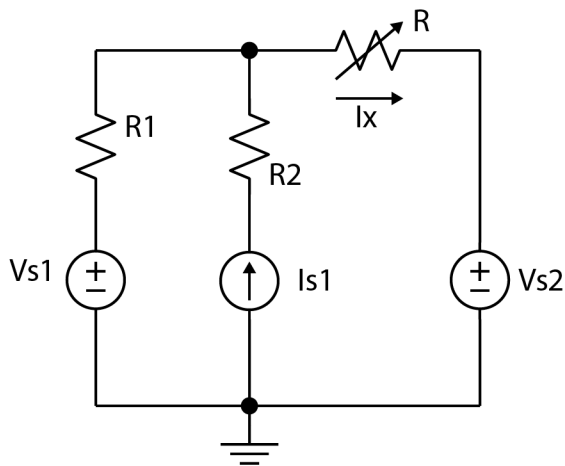


Problem 5: Find the equivalent resistance between points *a* and *b*. (15 points)

$R_1 = 5\ \Omega$ $R_2 = 10\ \Omega$ $R_3 = 40\ \Omega$ $R_4 = 20\ \Omega$ $R_5 = 25\ \Omega$

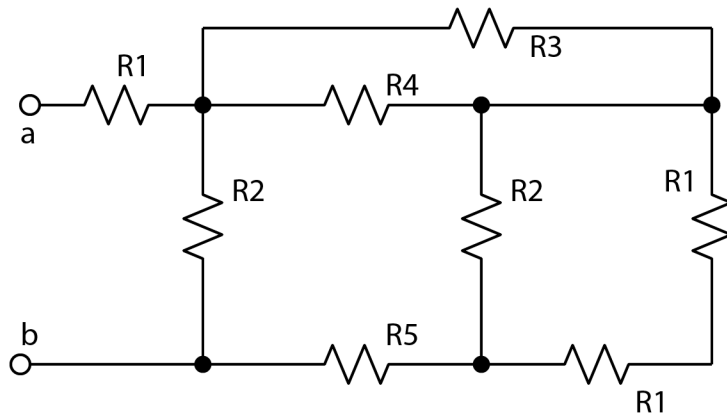


Problem 6: Find the equivalent resistance between points *a* and *b*. (15 points)

$R_1 = 20\ \Omega$ $R_2 = 10\ \Omega$

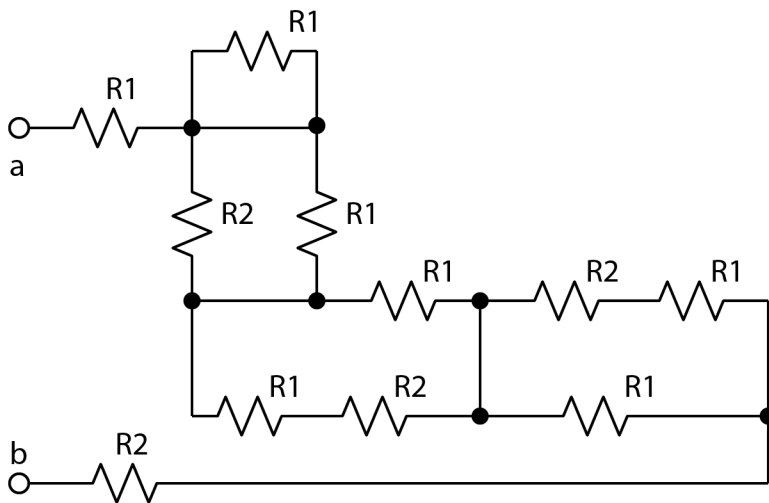

Problem 1

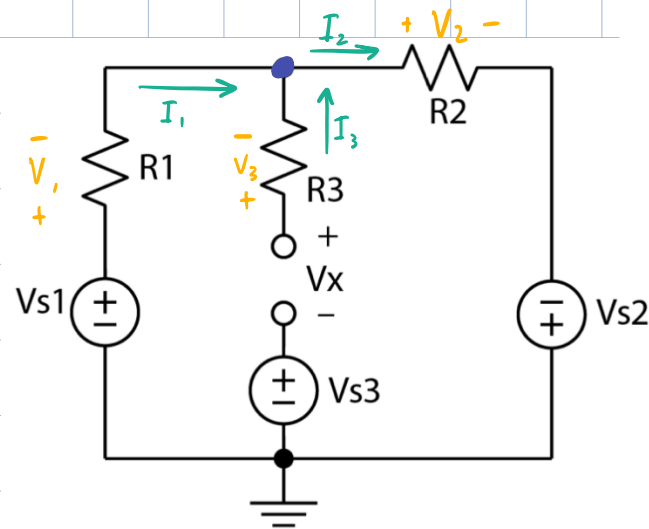

$$\text{KVL on } L_1: V_{s1} - V_1 + V_3 - V_x - V_{s3} = 0$$

$$\text{KVL on } L_2: V_{s2} + V_{s3} + V_x - V_3 - V_2 = 0$$


$$\text{KVL on } L_3: V_{s1} - V_1 - V_2 + V_{s2} = 0$$

Sub with Ohm's Law

$$V_{s1} - I_1 R_1 + I_3 R_3 - V_x - V_{s3} = 0$$

$$V_{s2} + V_{s3} + V_x - I_3 R_3 - I_2 V_2 = 0$$
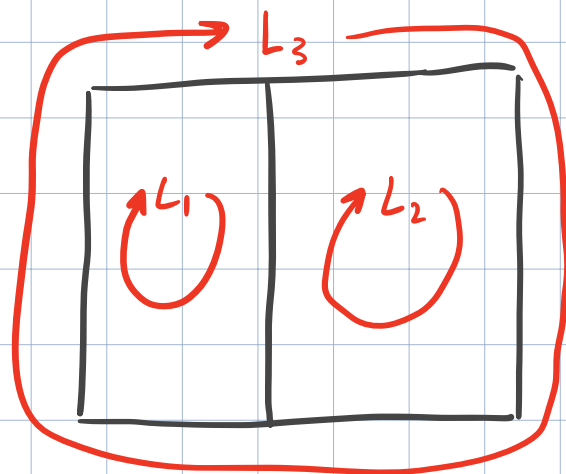
$$V_{s1} - I_1 R_1 - I_2 R_2 + V_{s2} = 0$$



Because of open circuit $I_3 = 0$ and $I_1 = I_2$

$$V_{s1} - I_1 R_1 - V_x - V_{s3} = 0 \quad (1)$$

$$V_{s2} + V_{s3} + V_x - I_1 R_2 = 0 \quad (2)$$

$$V_{s1} - I_1 R_1 - I_1 R_2 + V_{s2} = 0 \quad (3)$$

Solve (1) for I_1

$$I_1 R_1 = V_{s1} - V_x - V_{s3}$$

$$I_1 = \frac{V_{s1} - V_x - V_{s3}}{R_1}$$

(4)

Sub (4) into (2)

$$V_{s2} + V_{s3} + V_x - \left(\frac{V_{s1} - V_x - V_{s3}}{R_1} \right) R_2 = 0$$

$$V_{s2} + V_{s3} + V_x - \frac{V_{s1} R_2}{R_1} + \frac{V_x R_2}{R_1} + \frac{V_{s3} R_2}{R_1} = 0$$

$$V_x + \frac{V_x R_2}{R_1} = -V_{s2} - V_{s3} + \frac{V_{s1} R_2}{R_1} - \frac{V_{s3} R_2}{R_1}$$


$$V_x \left(1 + \frac{R_2}{R_1} \right) = -V_{s2} - V_{s3} + \frac{V_{s1} R_2}{R_1} - \frac{V_{s3} R_2}{R_1}$$

$$V_x = \frac{-V_{s2} - V_{s3} + \frac{V_{s1} R_2}{R_1} - \frac{V_{s3} R_2}{R_1}}{1 + \frac{R_2}{R_1}}$$

$$= \frac{-V_{s2} - V_{s3} + \frac{R_2}{R_1} (V_{s1} - V_{s3})}{1 + \frac{R_2}{R_1}}$$

$$= -4.75 \text{ V}$$

Problem 2

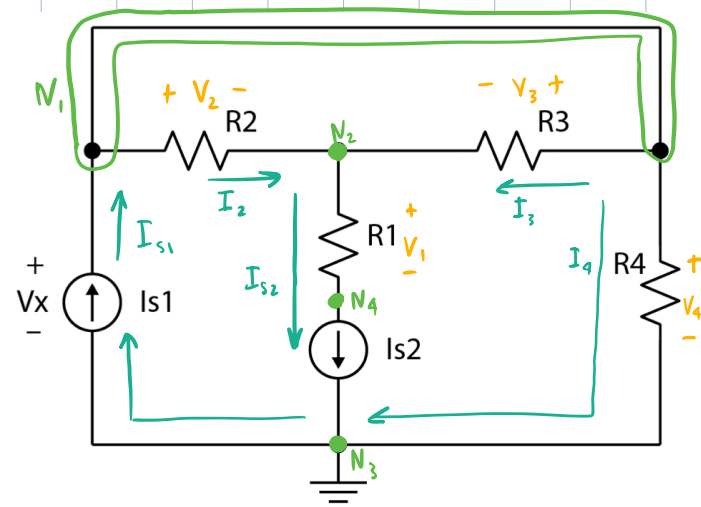

$$\text{Kcl at } N_1: I_{s1} = I_2 + I_3 + I_4 \quad (1)$$

$$\text{Kcl at } N_2: I_2 + I_3 = I_{s2} \quad (2)$$

$$\text{Kcl at } N_3: I_{s2} + I_4 = I_{s1} \quad (3)$$

$$\text{Kvl on } I_{s1} \rightarrow R_4: V_x - V_4 = 0 \quad (4)$$

Solve (4) using Ohm's Law and solve for V_x

$$V_x - R_4 I_4 = 0$$

$$V_x = R_4 I_4 \quad (5)$$

Solve for I_4 using (1) and (2)

$$I_{s1} = I_2 + I_3 + I_4$$

$$I_2 + I_3 = I_{s2}$$

$$I_{s1} = I_2 + I_3 + I_4$$

$$-I_{s2} = -I_2 - I_3$$


$$I_{s1} - I_{s2} = I_4 \quad (6)$$

Solve for V_x using (5) and (6)

$$V_x = R_4(I_{s1} - I_{s2})$$

$$= -5V$$

Problem 3a

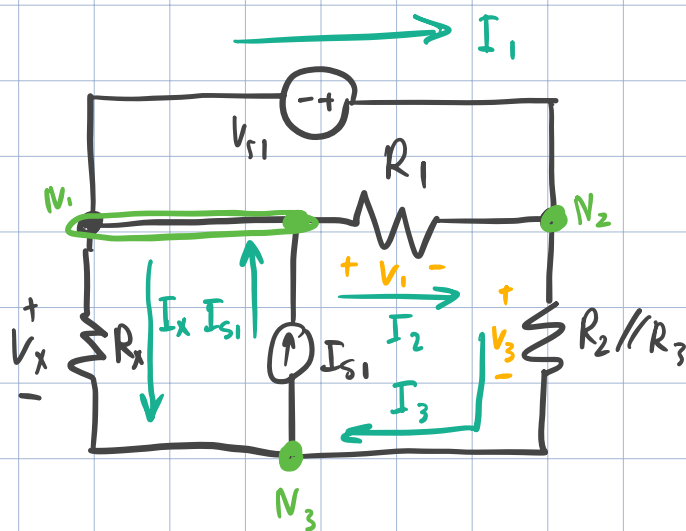

$$\text{Let } R_4 = R_2 \parallel R_3$$

3 back roads - 1 current source = 2 unknowns

$$\text{Kcl at } N_3 : I_{s1} = I_x + I_3$$

$$\text{Kcl at } N_2 : I_3 = I_2 + I_1$$

Solve for currents in terms of 2 unknowns

$$I_3 = I_{s1} - I_x$$

$$I_2 = I_x + I_{s1} - I_1$$

Find KVLs and write in terms of unknown currents

$$\text{Kvl on } V_x \rightarrow V_{s1} \rightarrow R_2 \parallel R_3 : V_x + V_{s1} - R_2 \parallel R_3 = 0$$

$$V_x + V_{s1} - I_3 R_4 = 0$$

$$V_x + V_{s1} - (I_s - I_x) R_4 = 0$$

$$I_x R_x + V_{s1} - (I_s - I_x) R_4 = 0$$

$$I_x R_x + V_{s1} - I_s R_4 + I_x R_4 = 0$$

$$I_x (R_x + R_4) = I_s R_4 - V_{s1}$$


$$I_x = \frac{I_s R_4 - V_{s1}}{R_x + R_4}$$

$$\frac{V_x}{R_x} = \frac{I_s R_4 - V_{s1}}{R_x + R_4}$$

$$V_x = R_x \frac{I_s R_4 - V_{s1}}{R_x + R_4}$$

$$= 76.575 \text{ V}$$

Problem 3b

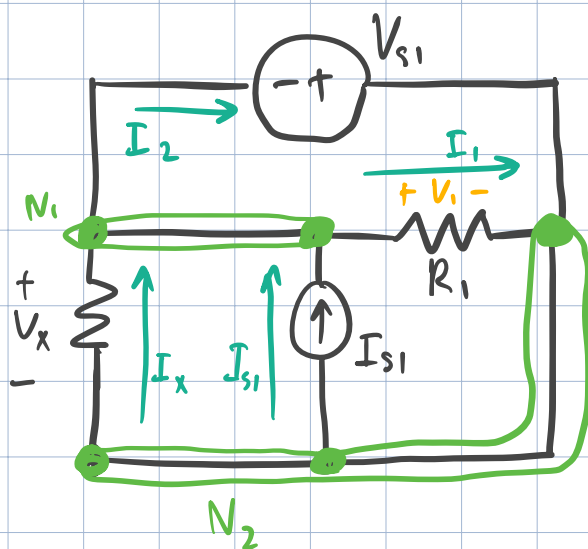


$$\text{Kvl on } V_x \rightarrow V_{s1}: V_x + V_{s1} = 0$$

$$V_x = -V_{s1}$$

$$= -5\text{V}$$

Problem 4a

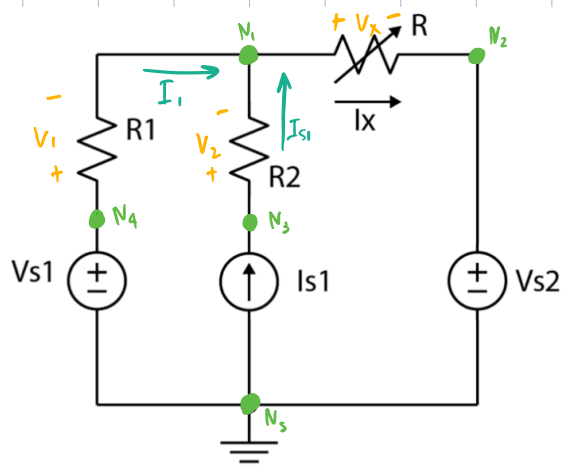

$$\text{KCL at } N_1: I_{s1} = I_1 + I_x \quad (1)$$

$$\text{KVL on } V_{s1} \rightarrow R_x \rightarrow V_{s2}: V_{s1} - V_1 - V_x - V_{s2} = 0 \quad (2)$$

$$I_x = I_{s1} - I_1$$

Solve (1) for I_x

$$I_x = I_{s1} + I_1 \quad (3)$$

Solve (2) for I_1

$$V_{s1} - I_1 R_1 - I_x R_x - V_{s2} = 0$$

$$I_1 R_1 = V_{s1} - I_x R_x - V_{s2}$$

$$I_1 = \frac{V_{s1} - I_x R_x - V_{s2}}{R_1} \quad (4)$$

Sub (4) into (3) and solve for I_x

$$I_x = I_{s1} + \frac{V_{s1} - I_x R_x - V_{s2}}{R_1}$$

$$I_x = I_{s1} + \left(\frac{V_{s1}}{R_1} - \frac{I_x R_x}{R_1} - \frac{V_{s2}}{R_1} \right)$$

$$I_x = I_{s1} + \frac{V_{s1}}{R_1} - \frac{I_x R_x}{R_1} - \frac{V_{s2}}{R_1}$$

$$I_x + \frac{I_x R_x}{R_1} = I_{s1} + \frac{V_{s1}}{R_1} - \frac{V_{s2}}{R_1}$$

$$I_x \left(1 + \frac{R_x}{R_1}\right) = I_{s1} + \frac{V_{s1}}{R_1} - \frac{V_{s2}}{R_1}$$

$$I_x = \frac{I_{s1} + \frac{V_{s1} - V_{s2}}{R_1}}{1 + \frac{R_x}{R_1}}$$

$$= \frac{\frac{I_{s1} R_1 + V_{s1} - V_{s2}}{R_1}}{\frac{R_1 + R_x}{R_1}}$$

$$= \frac{I_{s1} R_1 + V_{s1} - V_{s2}}{\cancel{R_1}} \cdot \frac{\cancel{R_1}}{R_1 + R_x}$$

$$= \frac{I_{s1} R_1 + V_{s1} - V_{s2}}{R_1 + R_x}$$

$$= \frac{5 + 10 - V_{s2}}{5 + R_x}$$

$$= \frac{15 - V_{s2}}{5 + R_x}$$

Problem 4b

$$\frac{1}{2} I_{s1} = \frac{15 - V_{s2}}{5 + R_x}$$

$$5 + R_x = \frac{15 - V_{s2}}{\frac{1}{2} I_{s1}}$$

$$R_x = \frac{15 - V_{s2}}{\frac{1}{2} I_{s1}} - 5$$

$$= 5 \Omega$$

Problem 4c

$$-\frac{1}{2} I_{s1} = \frac{15 - V_{s2}}{5 + R_x}$$




$$\left(-\frac{1}{2} I_{s1}\right)(5 + R_x) = 15 - V_{s2}$$





$$V_{s2} = 15 - \left(-\frac{1}{2} I_{s1}\right)(5 + R_x)$$

$$= 15 + \frac{1}{2} I_{s1} (5 + R_x)$$

$$= 20 \text{ V}$$

Problem 5

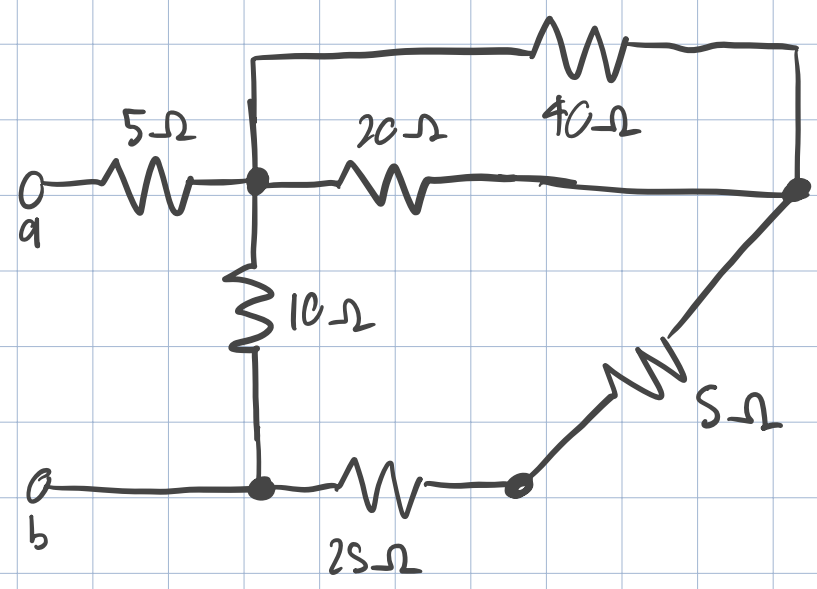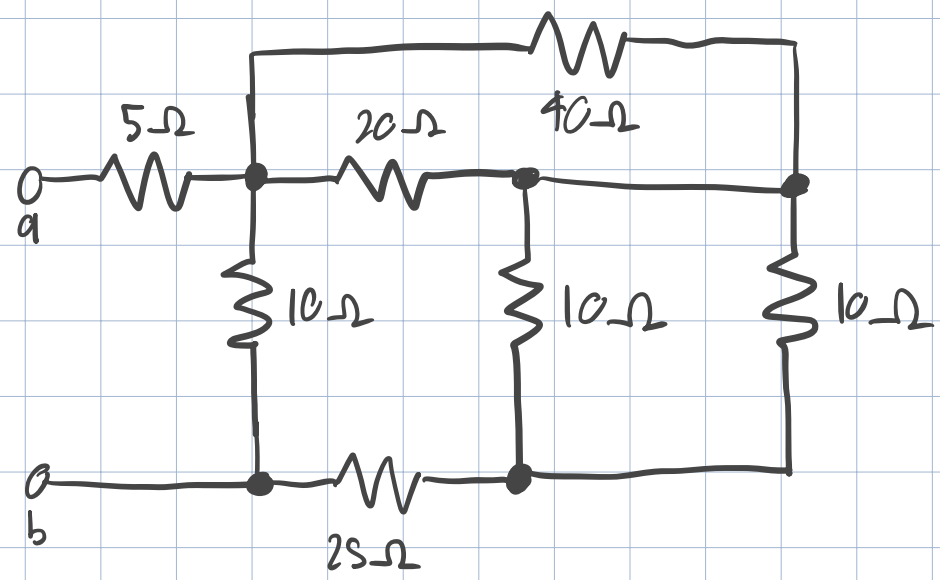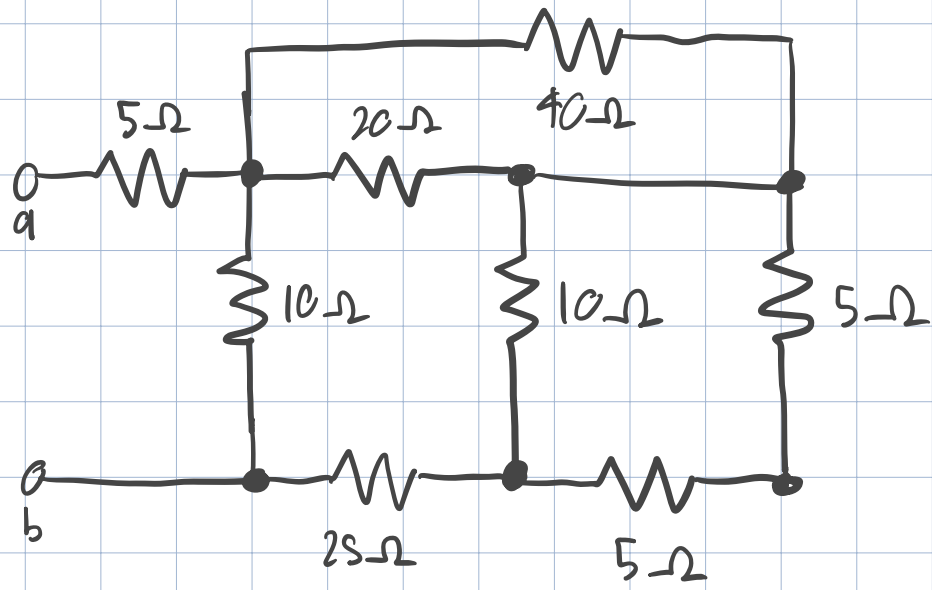

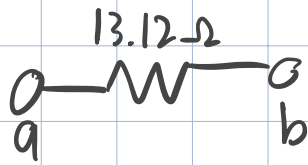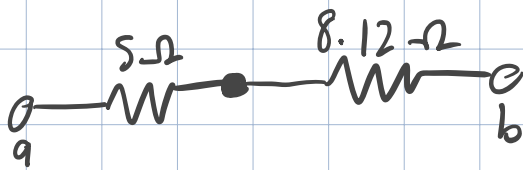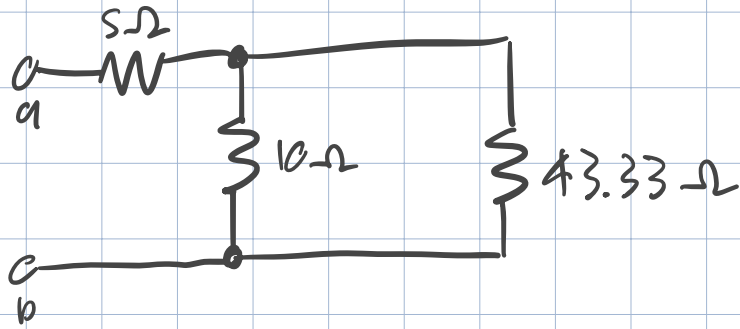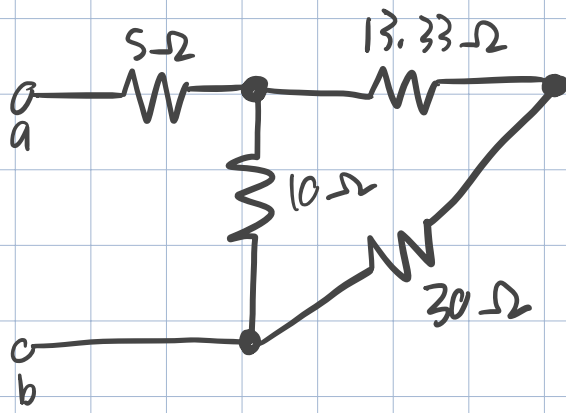

Problem 6

