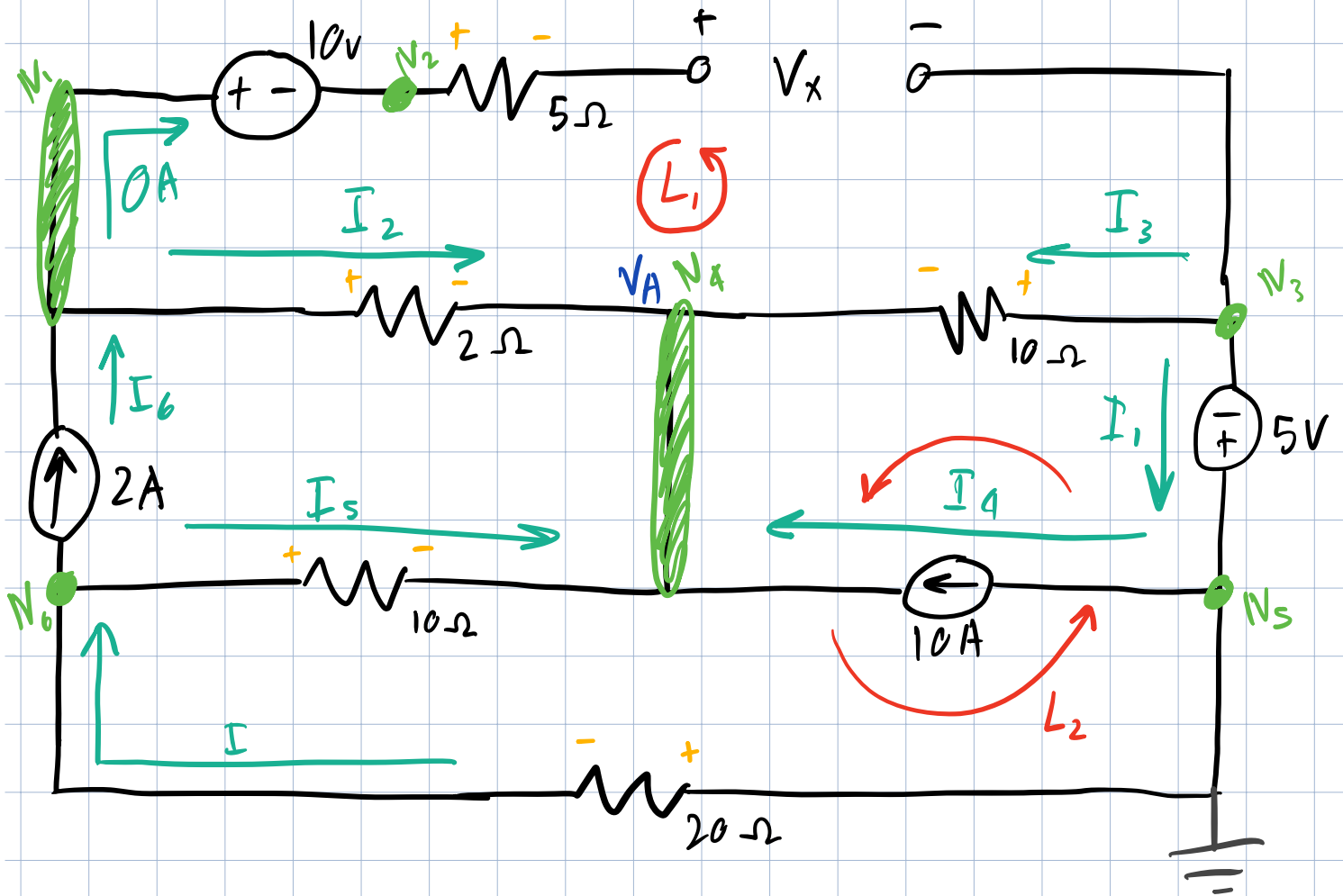


Problem One: Find  $V_x$ ,  $V_A$ , and  $I$



BCA: 3 backyards - 2 current sources = 1 unknown

NVA: 6 nodes - 1 ground - 2 voltage sources = 3 unknowns

Use Branch current analysis

Find Currents

$$I_6 = 2A$$

$$\text{Kcl at } N_1: I_2 = I_6$$

Currents

$$I_6 = 2A$$

$$I_2 = 2A$$

$$I_2 = I_6$$

$$= 2A$$

$$I_4 = 10A$$

$$\text{Kcl at } N_3: I_3 + I_1 = 0$$

$$I_3 = -I_1$$

$$\text{Kcl at } N_6: I = I_5 + I_6$$

$$I = I_5 + I_6$$

$$= I_5 + 2$$

$$\text{Kcl at } N_5: I_1 = I_4 + I$$

$$I_1 = I_4 + I$$

$$= 10 + (I_5 + 2)$$

$$= 12 + I_5$$

Solve for  $I_5$

KVL on  $L_2$ :

$$I_3 = -12 \cdot I_5$$

$$I_4 = 10A$$

$$I = I_5 + 2$$

$$I_1 = 12 + I_5$$

$$10I_5 + 20I - 5 - 10I_3 = 0$$

$$10I_5 + 20(I_5 + 2) - 5 - 10(-12 - I_5) = 0$$

$$2I_5 + 4(I_5 + 2) - 1 - 2(-12 - I_5) = 0$$

$$2I_5 + 4I_5 + 8 - 1 + 24 + 2I_5 = 0$$

$$8I_5 = -31$$

$$I_5 = -3.875$$

Solve for I

$$I = I_5 + 2$$

$$= -1.875 \text{ A}$$

Solve for  $V_A$

$$V_A = 0 - 5 - 10I_3$$

$$= -5 - 10(-12 + I_5)$$

$$= 76.25 \text{ V}$$

Solve for  $V_x$


Kvl on  $L_1$ :

$$-2I_2 + 10I_3 + V_x + 5 \cdot 0 + 10 = 0$$

$$-2(2) + 10(-12 + I_5) + V_x + 10 = 0$$

$$V_x = 75.25 \text{ V}$$

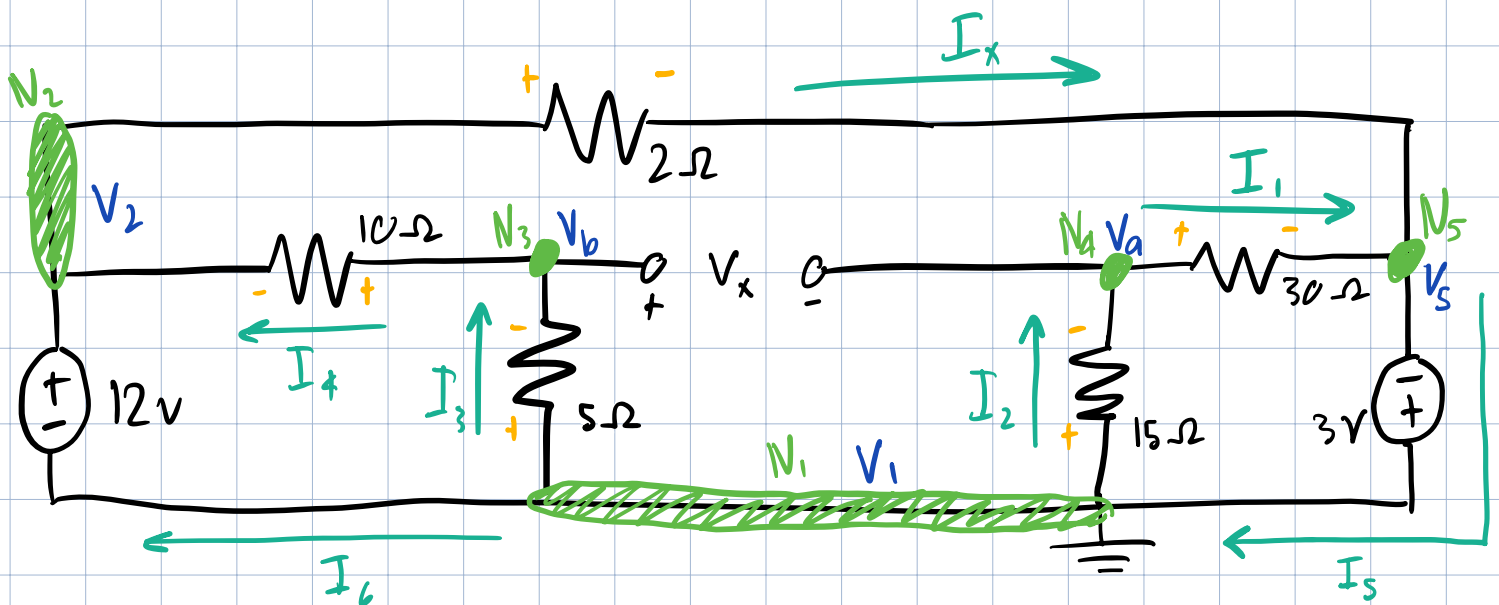Problem Two: Solve for  $V_x$  and  $I_x$



BCA: 3 backyards - 0 current sources = 3 unknowns

NVA: 5 nodes - 1 ground - 2 voltage sources = 2 unknowns

Use Node voltage analysis

Find voltages:

Voltages

Kcl at  $N_3$ :

$$I_4 = I_3$$

$$V_1 = 0 \text{ V}$$

$$\frac{V_b - V_2}{10} = \frac{0 - V_b}{5}$$

$$V_b - (12) = -2V_b$$

$$3V_b = 12$$

$$V_b = 4$$

Kcl at  $N_4$ :

$$I_1 = I_2$$

$$\frac{V_a - V_s}{30} = \frac{0 - V_a}{15}$$

$$V_a - V_s = -2V_a$$

$$3V_a = V_s$$

$$V_a = \frac{-3}{3}$$

$$= -1V$$

$$V_2 = 12V$$

$$V_s = -3V$$

$$V_b = 4V$$

$$V_a = -1V$$

Solve for  $V_x$


$$V_x = V_b - V_a$$

$$= 5V$$

Solve for  $I_x$  over the  $2\Omega$  resistor

$$\begin{aligned} I_x &= \frac{V_2 - V_5}{2} \\ &= \frac{12 + 3}{2} \\ &= \frac{15}{2} \text{ V} \end{aligned}$$

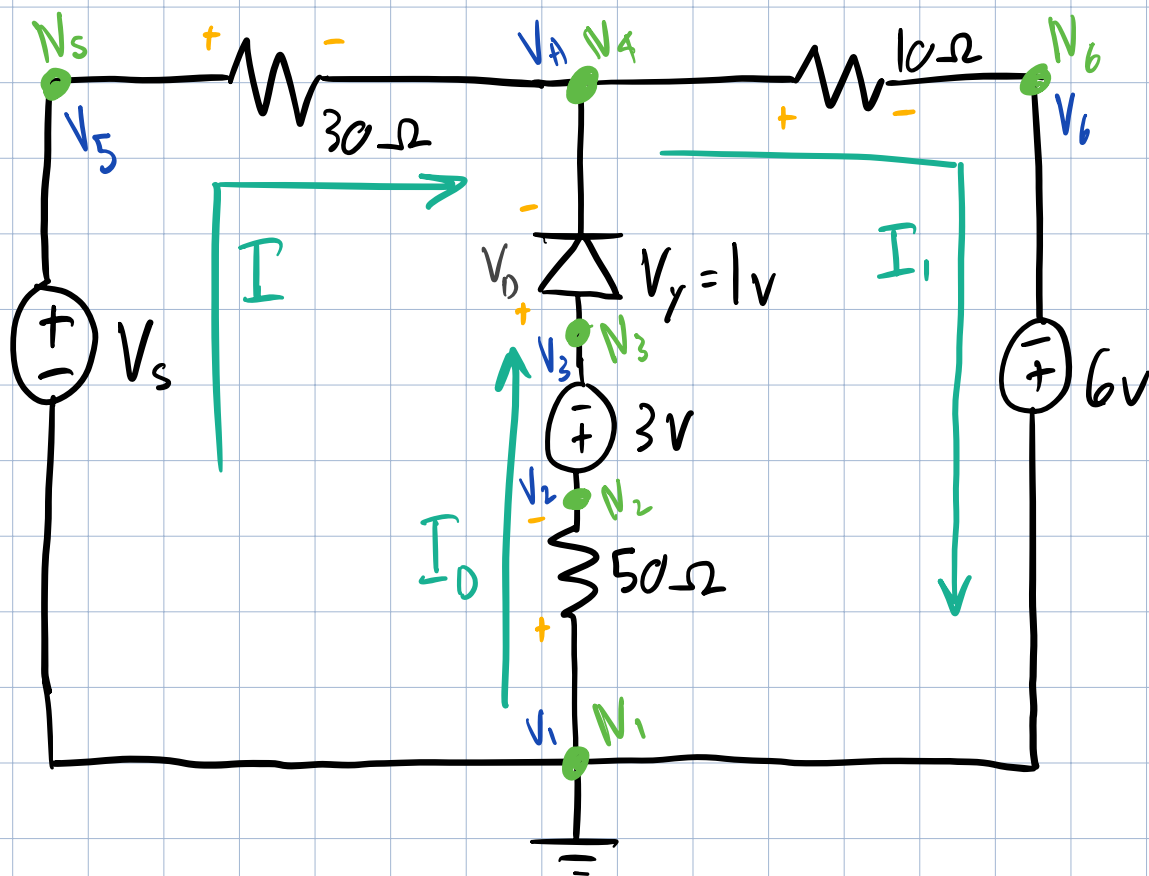Problem 3: Find  $V_s$  so the diode is ON and OFF. Find  $I$  and  $V_A$



Solve with diode OFF

Use Node Voltage Analysis because it's easier

NVA: 6 Nodes - 1 ref - 3 voltage sources = 2 unknowns

Solve for voltages

Known Voltages

Kcl at  $N_4$ :

$$I = I_1$$

$$\frac{V_s - V_A}{30} = \frac{V_A - V_6}{10}$$

$$V_s - V_A = 3(V_A + 6)$$

$$V_s - V_A = 3V_A + 18$$

$$-4V_A = 18 - V_s$$

$$V_A = \frac{V_s - 18}{4}$$

---

Kcl at  $N_2$

$$I_D = I_D$$

$$0 = \frac{V_1 - V_2}{50}$$

$$0 = 0 - V_2$$

$$V_2 = 0$$

---

$$V_3 = V_2 - 3$$

$$V_1 = 0V$$

$$V_5 = V_s$$

$$V_6 = -6V$$

$$V_A = \frac{V_s - 18}{4}$$

$$V_2 = 0V$$

$$V_3 = -3V$$

$$= -3V$$

Solve for  $V_D > V_Y$

$$V_D = V_3 - V_A$$

$$V_D = -3 - \frac{V_s - 18}{4}$$

Decide on when  $V_D > V_Y$

$$-3 - \frac{V_s - 18}{4} > 1$$

$$-12 - V_s + 18 > 4$$

$$-V_s > -2$$

$$V_s < 2V$$

Solve for  $I$  over the  $30\Omega$  resistor

$$I = \frac{V_s - V_A}{30}$$

$$= \frac{V_s - \frac{V_s - 18}{4}}{30}$$


$$= \frac{\frac{4V_s - V_s + 18}{4}}{30}$$

$$= \frac{\cancel{3}V_s + \cancel{18}^6}{4} \cdot \frac{1}{\cancel{30}^{10}}$$



$$= \frac{V_s + 6}{40}$$

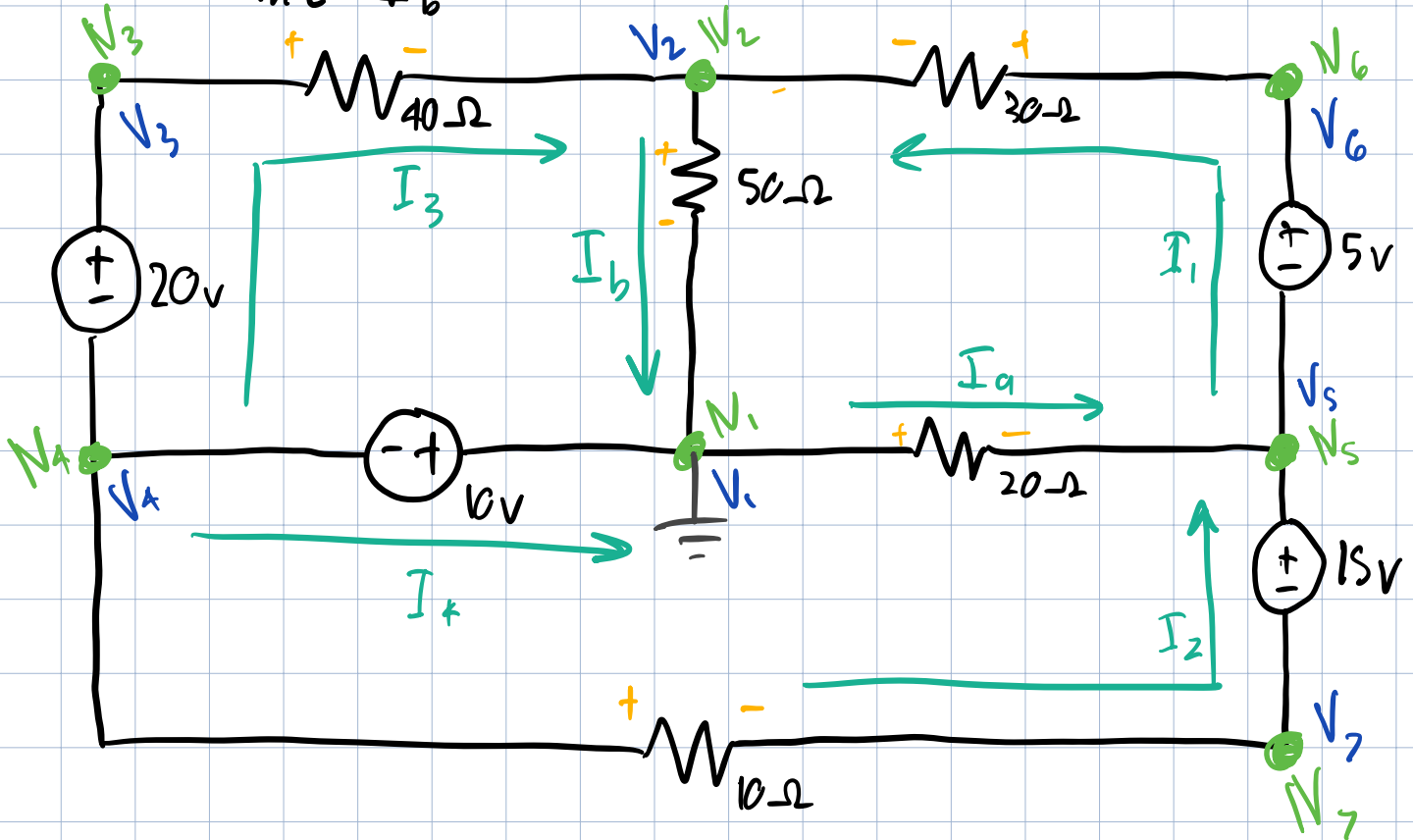Problem 4: Determine all node voltages in terms of  $I_a$  and  $I_b$



Use Node Voltage Analysis

7 Nodes - 1 Ref - 4 voltage sources = 2 unknowns

Find voltages

$$20 I_a = V_1 - V_5$$

$$V_5 = -20 I_a$$

Known Voltages

$$V_1 = 0 \text{ V}$$

$$V_4 = -10 \text{ V}$$

$$V_3 = 10 \text{ V}$$

$$50 I_b = V_2 - V_1$$

$$V_2 = 50 I_b$$


$$V_5 = -20 I_a$$

$$V_6 = -20 I_a + 5$$

$$V_7 = -20 I_a - 15$$

$$V_2 = 50 I_b$$

## Problem 5

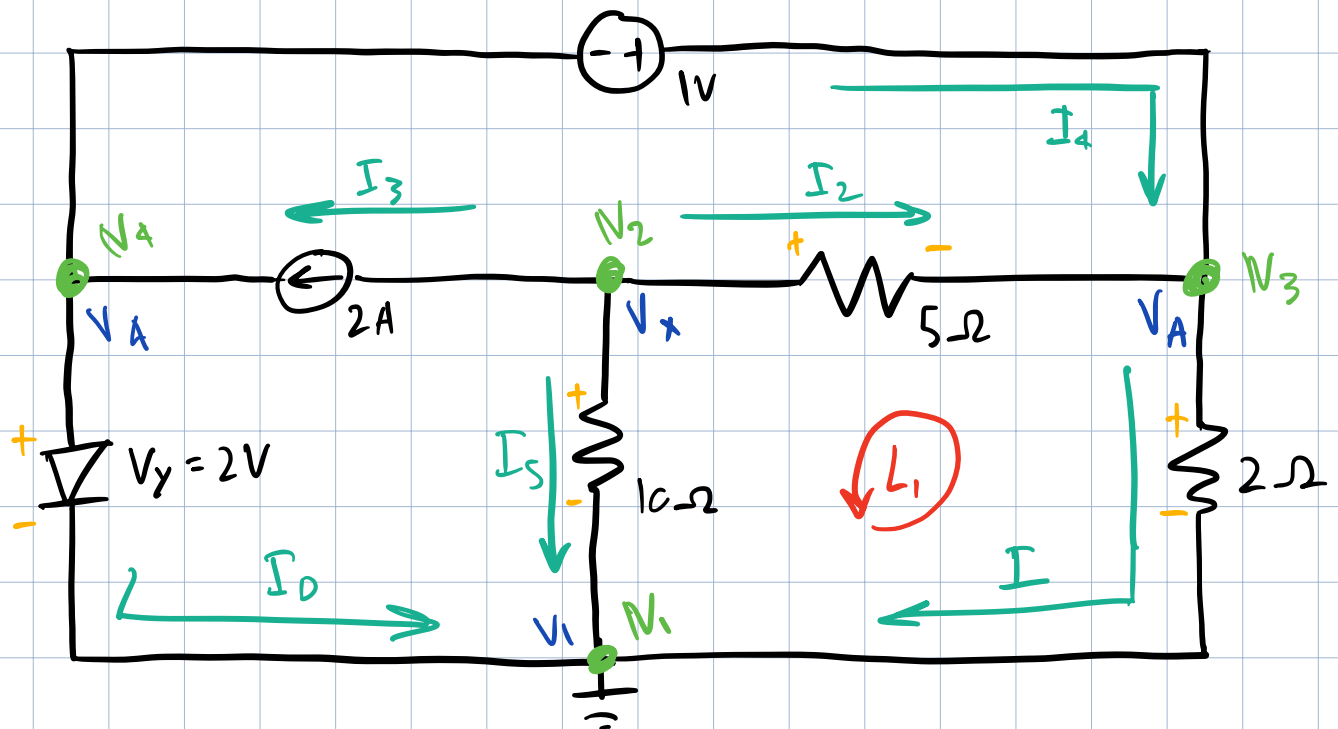

Solve assuming the diode is ON

BCA: 3 backgrounds - 1 current source = 2 unknowns

NVA: 4 nodes - 1 ref - 2 voltage sources = 1 unknown

Use Node Voltage Analysis

Find Voltages

Kcl at  $N_2$

$$0 = I_3 + I_2 + I_5$$

$$0 = 2 + \frac{V_x - V_A}{5} + \frac{V_x - V_1}{10}$$

$$0 = 20 + 2(V_x - 3) + (V_x - V_1)$$

$$0 = 20 + 2V_x - 6 + V_x$$

$$-3V_x = 14$$

$$V_x = -\frac{14}{3}$$

Solve for  $I_D$

Kcl at  $N_1$ :

$$I_D + I_5 + I = 0$$

$$I_D + \frac{V_x - V_1}{10} + \frac{V_A - V_1}{2} = 0$$

$$10I_D + \left(-\frac{14}{3} - 0\right) + 5(3 - 0) = 0$$

$$10I_D = -15 + \frac{14}{3}$$

$$I_D = -\frac{31}{30} \text{ A}$$

Voltages

$$V_1 = 0 \text{ V}$$

$$V_4 = 2 \text{ V}$$

$$V_A = 3 \text{ V}$$

$$V_x = -\frac{14}{3}$$

Diode is CFF

Solve assuming diode is CFF

BCA: 2 backwards - 1 current source = 1 unknown

NVA: 4 Nodes - 1 Ref - 1 voltage source = 2 unknowns

Use Branch Current Analysis

Solve for currents

Currents

$$\text{Kcl at } N_1:$$

$$I_s = I$$

$$I_D = 0A$$

$$I_s = -I$$

$$\text{Kcl at } N_2:$$

$$I_3 + I_2 + I_s = 0$$

$$I_3 = 2A$$

$$2 + I_2 - I = 0$$

$$I_2 = I - 2$$

$$I_2 = I - 2$$

$$I_4 = 2A$$

$$\text{Kvl at } N_3:$$

$$I_4 + I_2 = I$$

$$I = \frac{10}{12} A$$

$$I_4 + I - 2 = I$$

$$I_4 = 2$$

Kvl on  $L_1$ :

$$2I + 5I_2 - 10I_5 = 0$$

$$2I + 5(I - 2) - 10(-I) = 0$$

$$2I + 5I - 10 + 10I = 0$$

$$17I = 10$$

$$I = \frac{10}{17}$$

Solve for  $V_D$

Kcl at  $N_1$ :

$$I_D + I_5 + I = 0$$

$$(V_4 - V_1) + I_5 + I = 0$$

$$V_4 = -I_5 + I$$

$$= 2I$$

$$= \frac{20}{17} \text{ V}$$

Diode must be OFF