


## Homework 4

Clearly describe the reasoning behind the work done in each problem.

SOLVE 5 OF ANY OF THE FOLLOWING PROBLEMS.


**Problem 1:** (20 points)

Solve for the capacitor's current and voltage,  $i_c$  and  $v_c$ , at  $t = 0^-$ ,  $t = 0^+$  and  $t = \infty$ .

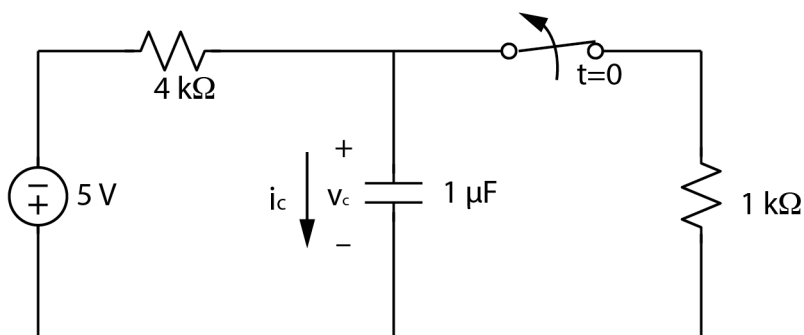


**Problem 2:** (20 points)

Solve for  $v_c$ ,  $i_c$  and  $i_s$  at  $t = 0^-$ ,  $t = 0^+$  and  $t = \infty$ . Explain whether the capacitor is charging or discharging.

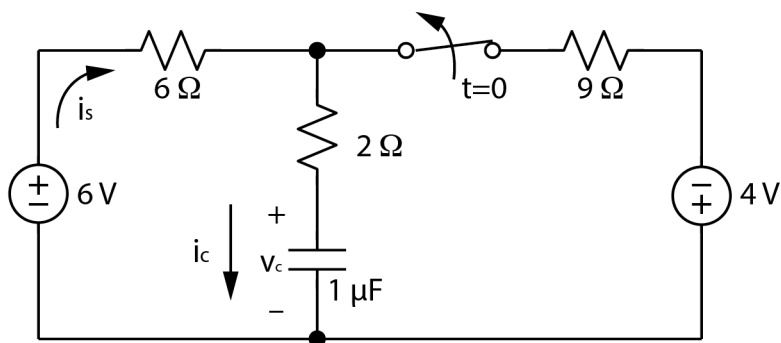


**Problem 3:** (20 points)

Consider the two-position switch in the circuit, which has been in position a for a long time. At time  $t=0$  the switch moves to position b. Determine the time for the capacitor to discharge to 2V and calculate the current at that time.

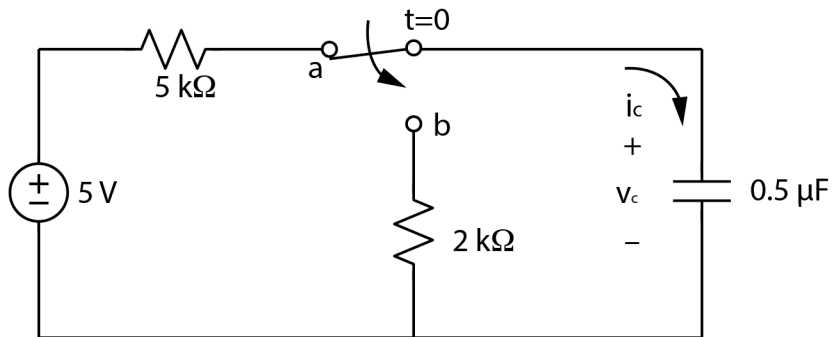


**Problem 4:** (20 points)

Solve for  $i_x$  at  $t = 0^-$ ,  $t = 0^+$  and  $t = \infty$ .

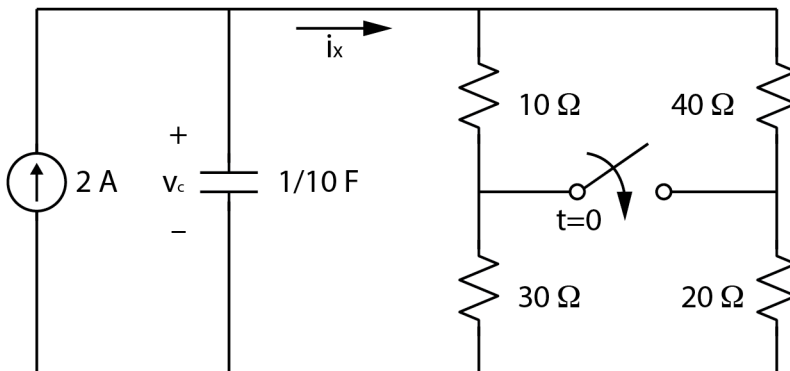


**Problem 5:** (20 points)

Solve for  $v_x$  and  $i_c$  at  $t = 0^-$ ,  $t = 0^+$  and  $t = \infty$ .

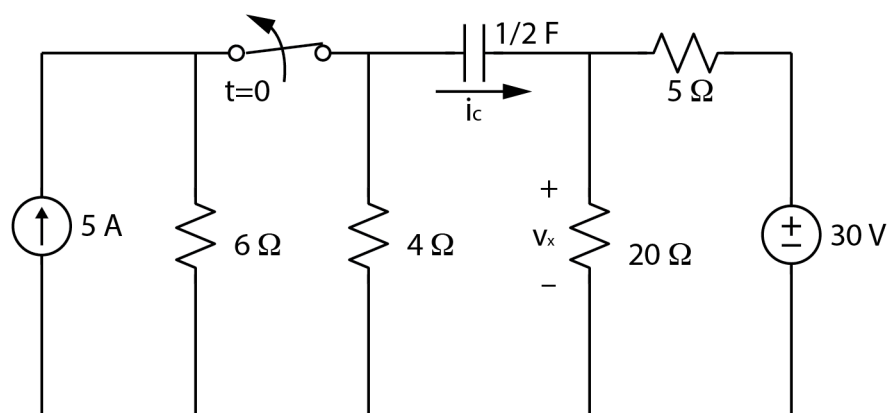


**Problem 6:** (30 points)

Solve for  $v_x$  at  $t = 0^-$ ,  $t = 0^+$  and  $t = \infty$ .

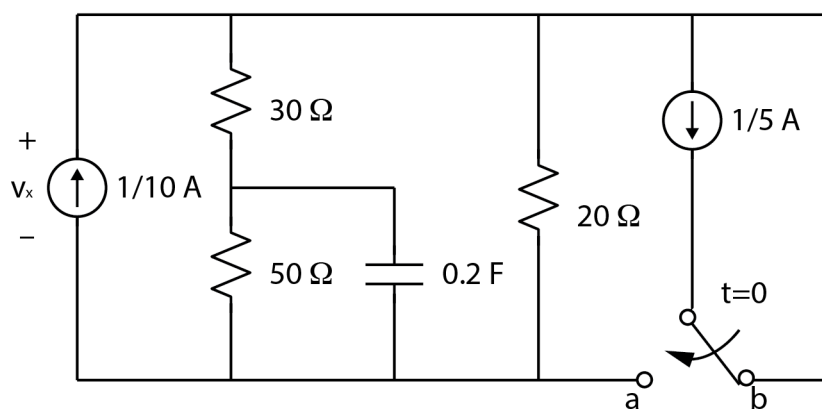


**Problem 7: (20 points)**

Solve for  $i_c$  at  $t = 0^-$ ,  $t = 0^+$  and  $t = \infty$ .

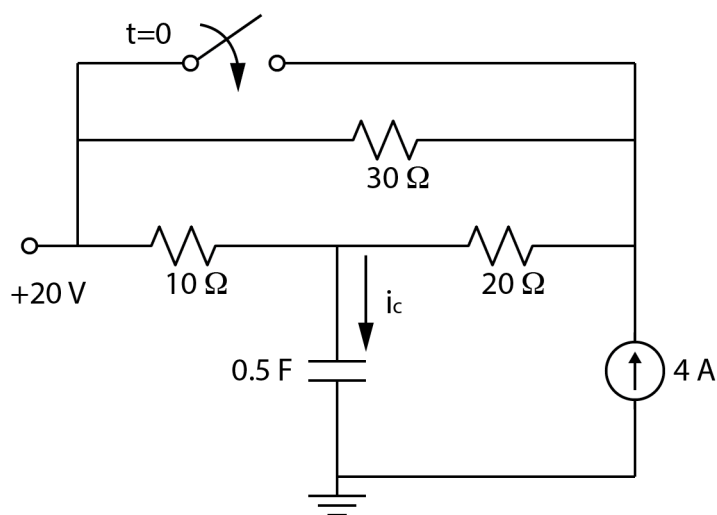

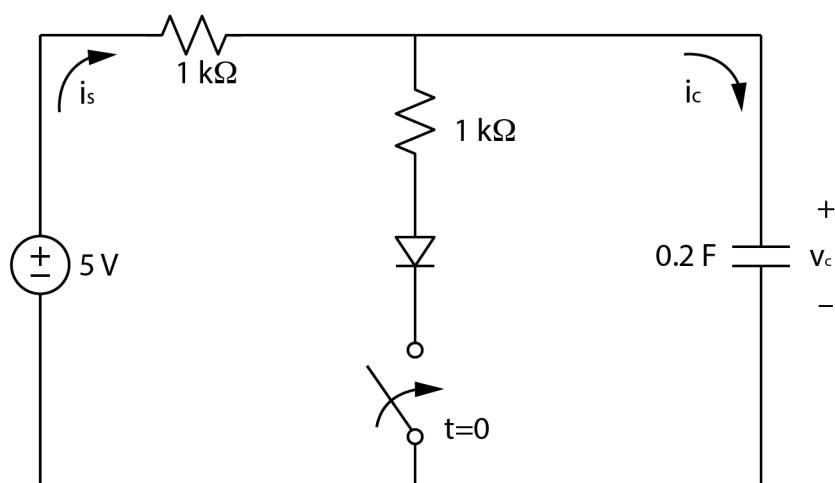
**Problem 8: (30 points)**

Solve for  $v_c$ ,  $i_c$  and  $i_s$  at  $t = 0^-$ ,  $t = 0^+$  and  $t = \infty$ .  $V_\gamma = 1$  V.



## Problem 1a

When  $t = 0^-$

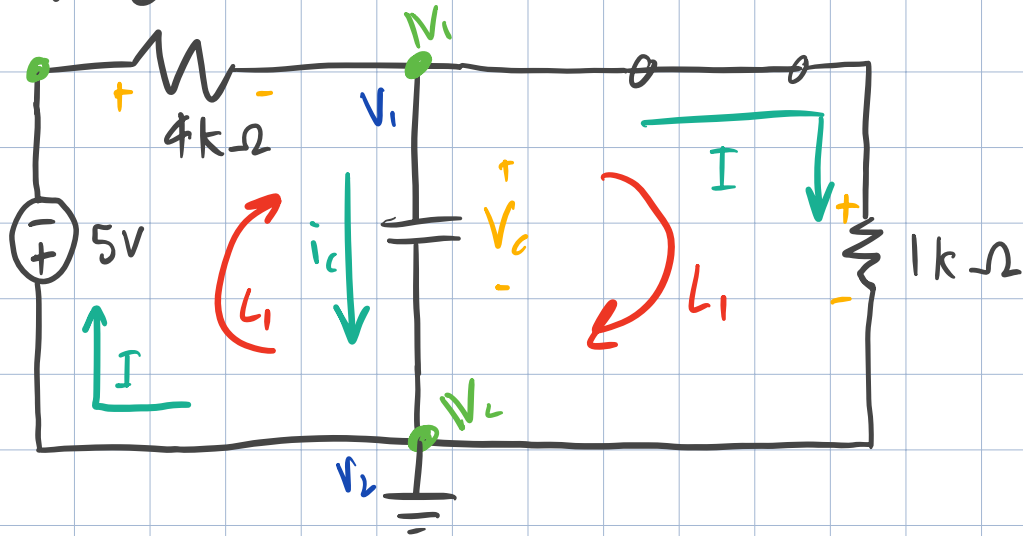

$$i_c = 0 \text{ A}$$

$$V_c = -1 \text{ V}$$

Solve for  $V_c$

$$V_2 = 0$$

$$V_1 = -5 - 4000 I$$

Solve for  $I$

KVL on  $L_1$ :

$$5 + 1000 I + 4000 I = 0$$

$$5000 I = -5$$

$$I = \frac{-1}{1000} \text{ A}$$


$$V_1 = -5 + 4$$

$$= -1 \text{ V}$$

$$V_c = V_1 - V_2$$

$$= -1 \text{ V}$$

When  $t = 0^+$

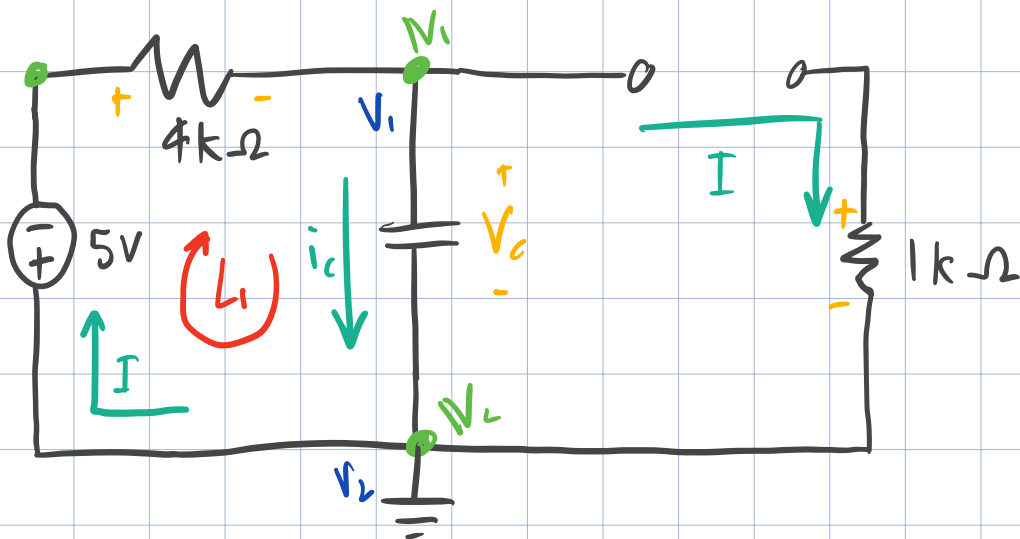

$$i_c = -\frac{1}{1000} \text{ A}$$

$$V_c = -1 \text{ V}$$

Solve for I

$$I = i_c$$

KVL on  $L_1$


$$5 + V_c + 4000 I = 0$$

$$5 - 1 + 4000 I = 0$$

$$I = -\frac{4}{4000} \text{ A}$$

$$= -\frac{1}{1000} \text{ A}$$

When  $t = \infty$

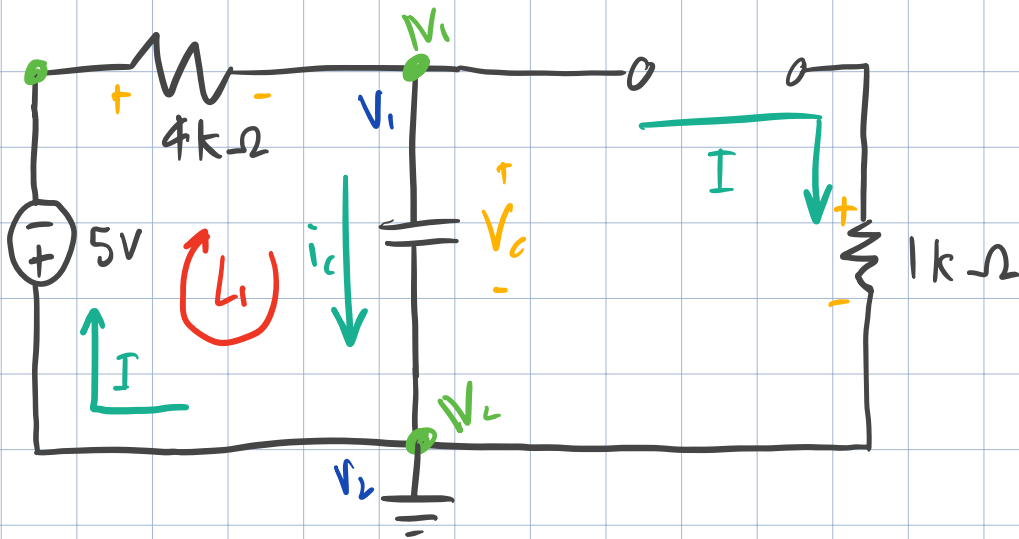

$$i_c = 0 \text{ A}$$

$$V_c = -5 \text{ V}$$

Solve for  $V_c$


KVL on  $L_1$

$$5 + V_c + 4000 I = 0$$

$$V_c = -5V$$

## Problem Two

When  $t = 0^-$

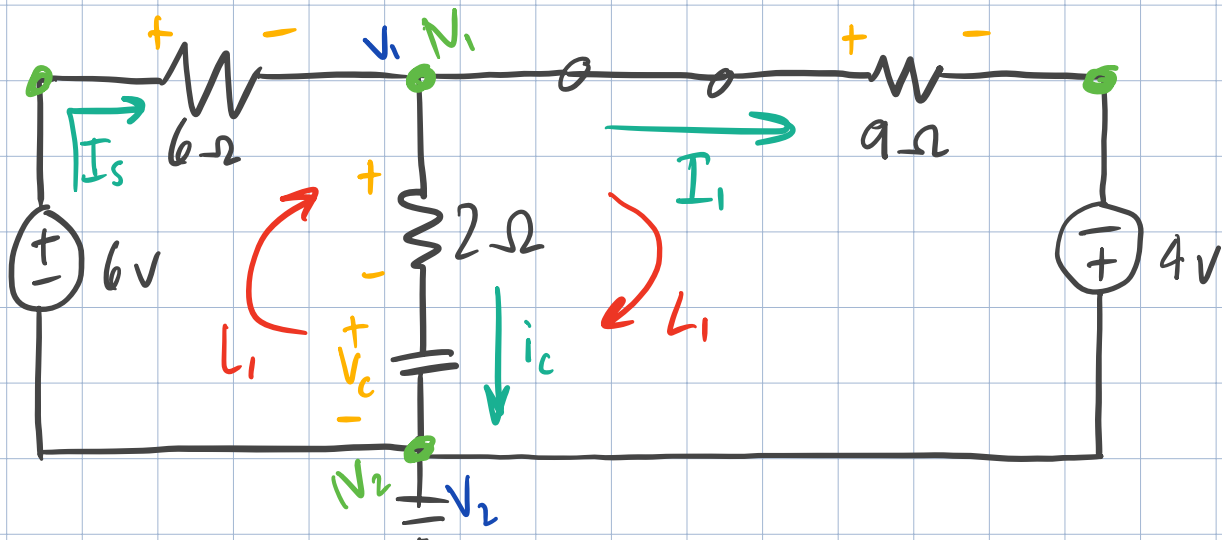

$$i_c = 0A$$

$$V_c = 2V$$

$$I_s = \frac{2}{3}A$$

Solve for  $I_s$

$$I_s = I_1$$

Kvl on  $L_1$

$$6 - 6I - 9I + 4 = 0$$

$$-15I = -10$$



$$I = \frac{10}{15} = \frac{2}{3} \text{ A}$$

Solve for  $V_c$

$$V_c = V_1 - V_2$$

$$V_2 = 0 \text{ V}$$


$$V_1 = 6 - 6I$$

$$= 6 - \frac{12}{3}$$

$$= 6 - 4$$

$$= 2 \text{ V}$$

When  $t = 0^+$

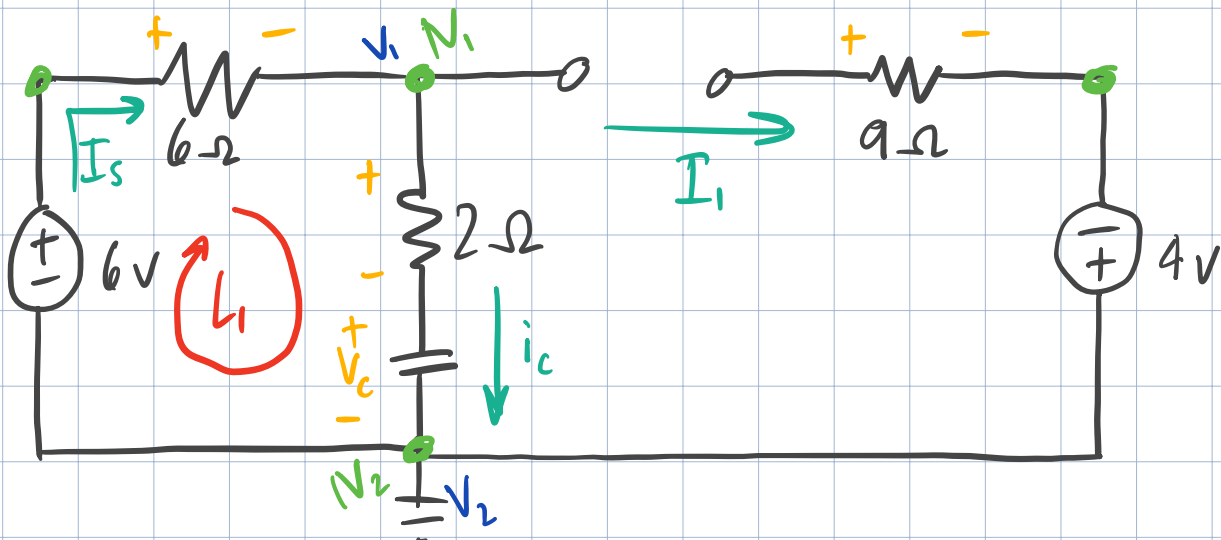

$$i_c = \frac{1}{2} \text{ A}$$

$$V_c = 2V$$

$$I_s = \frac{1}{2}A$$

Solve for  $i_c$

$$I_s = i_c$$

Kcl on  $L_1$


$$6 - 6I_s - 2I_s - 2 = 0$$

$$4 - 8I_s = 0$$

$$I_s = \frac{4}{8}$$

$$= \frac{1}{2}A$$

When  $t = \infty$

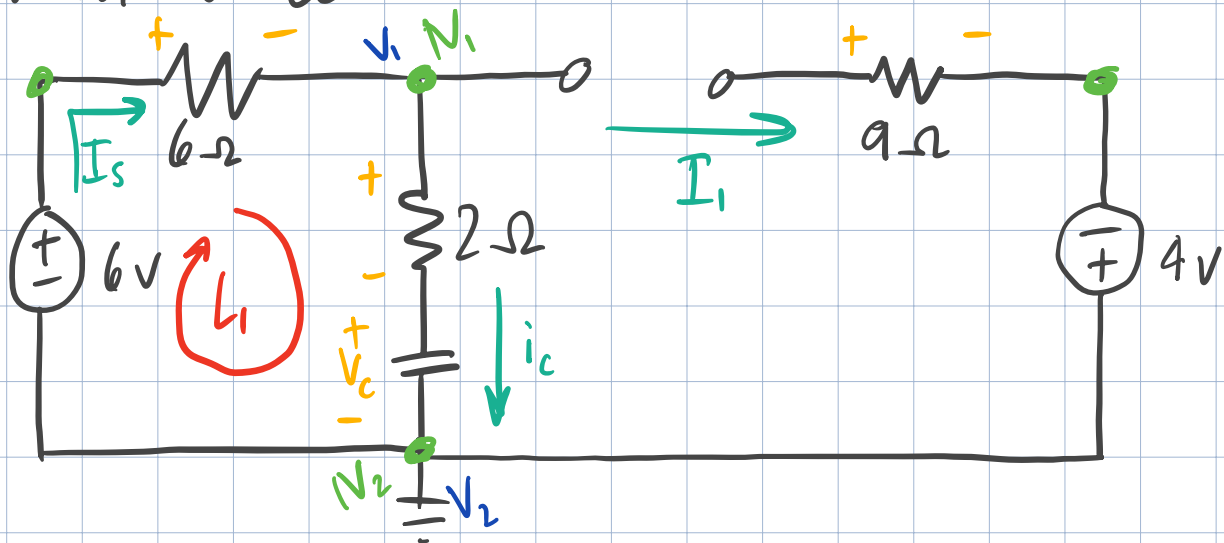

$$i_c = 0A$$

$$V_c = 6V$$


$$I_s = 0A$$

At  $t=0^-$  the capacitor is charged and not charging or discharging.

At  $t=0^+$  the capacitor is charging because the current flow through the capacitor is positive.

At  $t=\infty$  the capacitor is charged and not charging or discharging.

### Problem Three

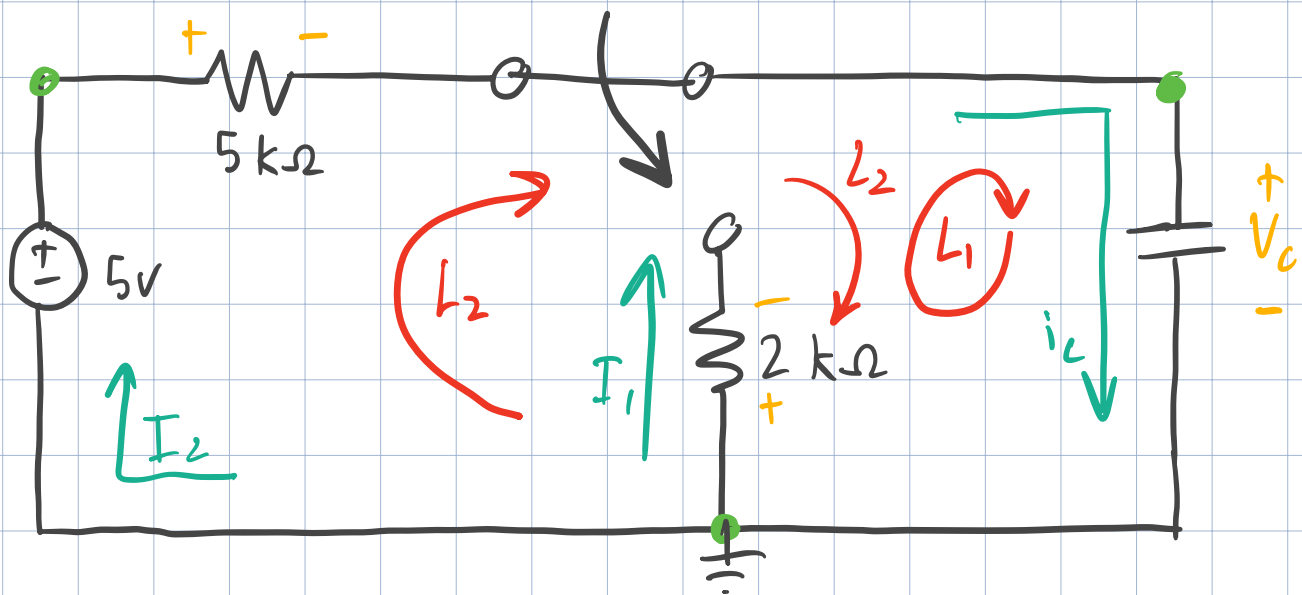

$$\text{At } t=0^- : V_c = 5V$$

$$\text{When } 0^+ < t < \infty$$

$$Kcl \text{ on } L_1$$

$$V_c + 2000 i_c = 0$$

$$V_c + 2000 \frac{dq}{dt} = 0$$

$$V_c + 2000 C \frac{dV_c}{dt} = 0$$

Differential Equation Solving

$$V_c = V_c(0^+) e^{-\frac{t}{RC}}$$

$$\frac{V_c}{V_c(0^+)} = e^{-\frac{t}{RC}}$$

$$-\frac{t}{RC} = \ln\left(\frac{V_c}{V_c(0^+)}\right)$$

$$t = -RC \ln\left(\frac{V_c}{V_c(0^+)}\right)$$

$$= -(2000)(0.5e-6) \ln\left(\frac{V_c}{5}\right)$$

Solve for t when  $V_c = 2v$

$$t = -(2000)(0.5e-6) \ln\left(\frac{2}{5}\right)$$

$$= 9.1629e-4 s$$

Solve for  $i_c$  at  $t = 9.1629e-4 s$

Kvl on  $h_1$

$$2000i_c - V_c(t) = 0$$



$$i_c = \frac{V_c(t)}{2000}$$

$$= \frac{2}{2000}$$

$$= \frac{1}{1000} \text{ A}$$



## Problem Four

When  $t = 0^-$

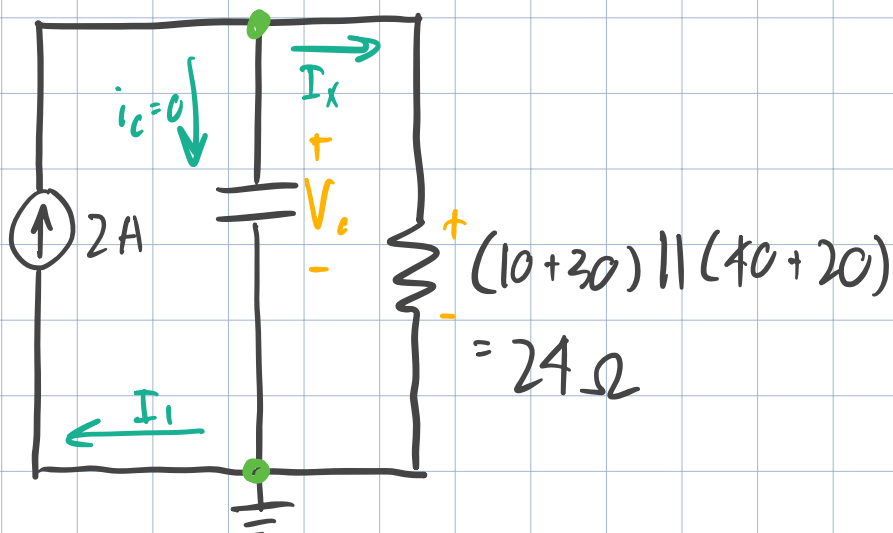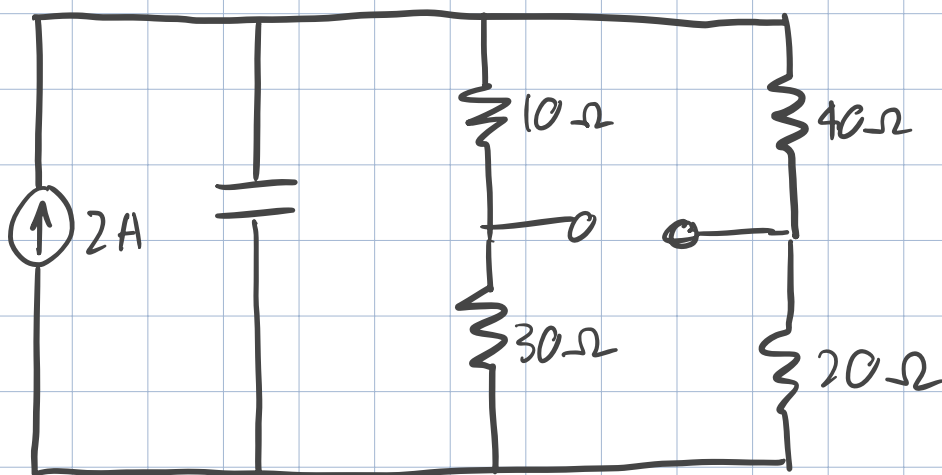

$$I_x = 2A$$

When  $t = 0^+$

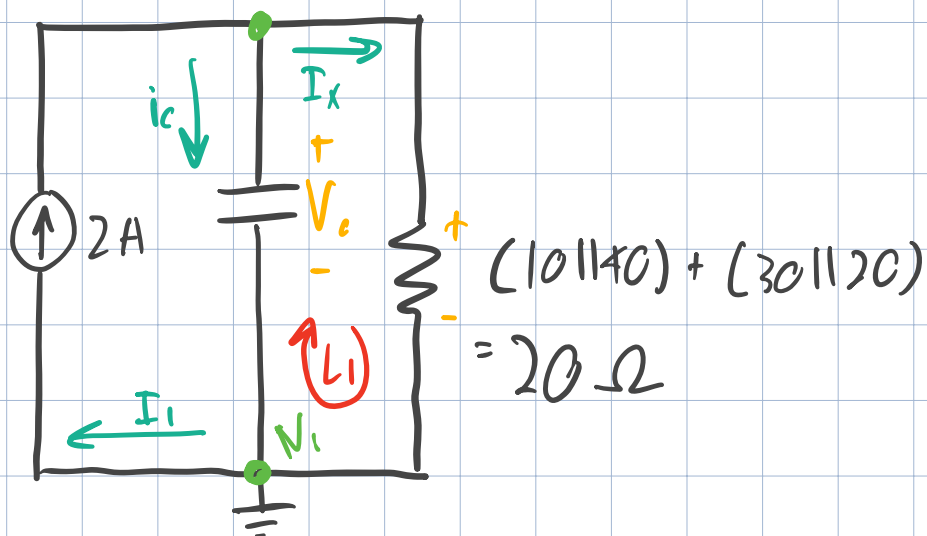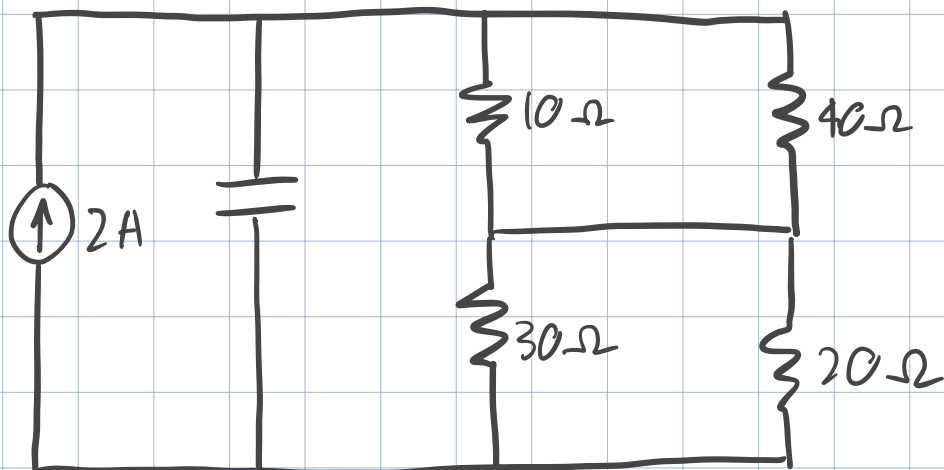

Solve for  $I_x$

Kvl on  $L_1$

$$V_c(0^+) - 20I_x = 0$$

$$V_c(0^-) - 20I_x = 0$$

$$V_c(0^-) = 48V$$

$$48 - 20I_x = 0$$

$$I_x = \frac{48}{20} \text{ A}$$

$$= \frac{12}{5} \text{ A}$$


When  $t = \infty$

$$I_x = 2 + i_c(\infty)$$

$$= 2 \text{ A}$$

## Problem Five

When  $t = 0^-$

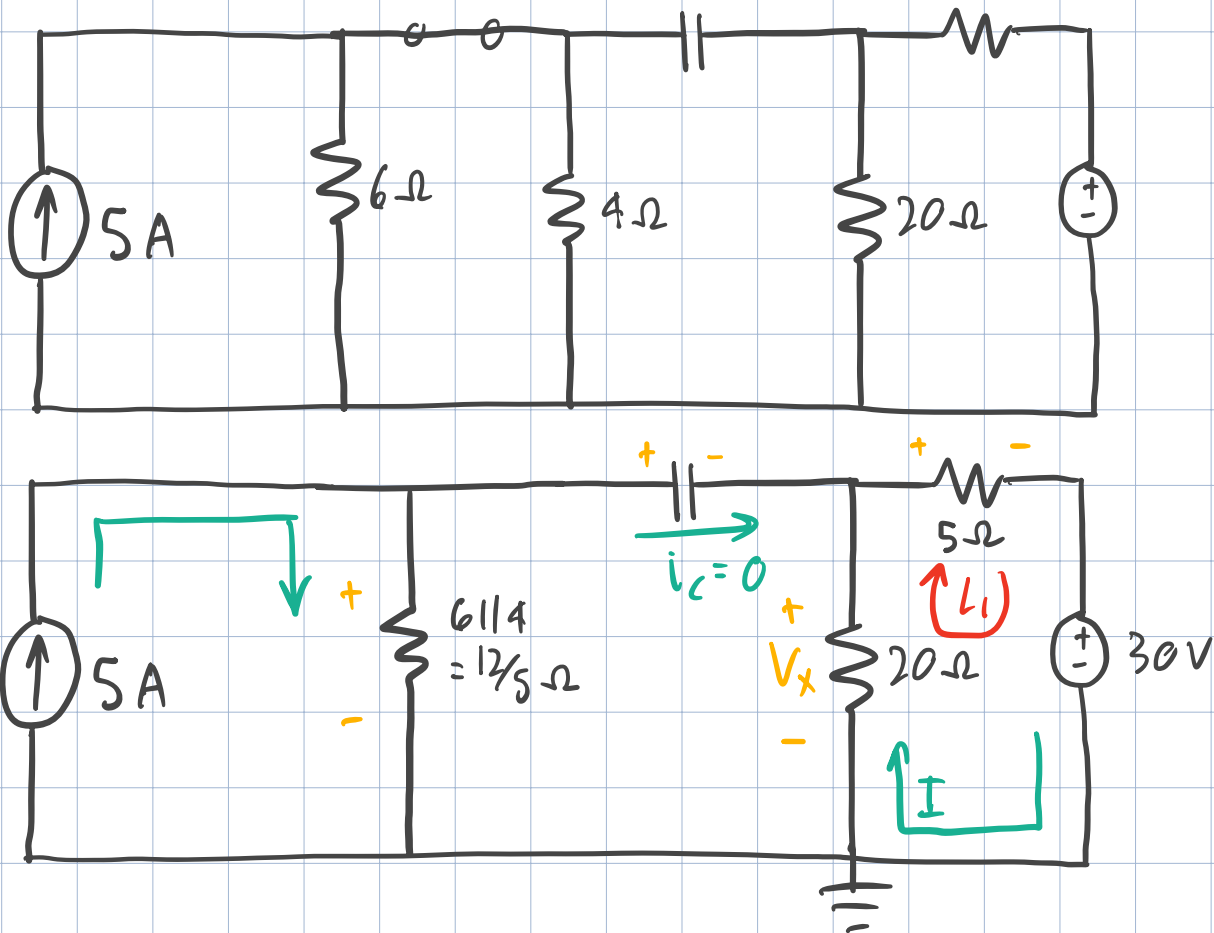

Solve for  $V_x$

$$\text{Kvl on } L_1$$

$$20I + 5I - 30 = 0$$

$$25I = 30$$


$$I = \frac{6}{5} \text{ A}$$

$$V_x = IR$$

$$= \frac{6}{5} \cdot 20$$

$$= 24 \text{ V}$$

When  $t = 0^+$

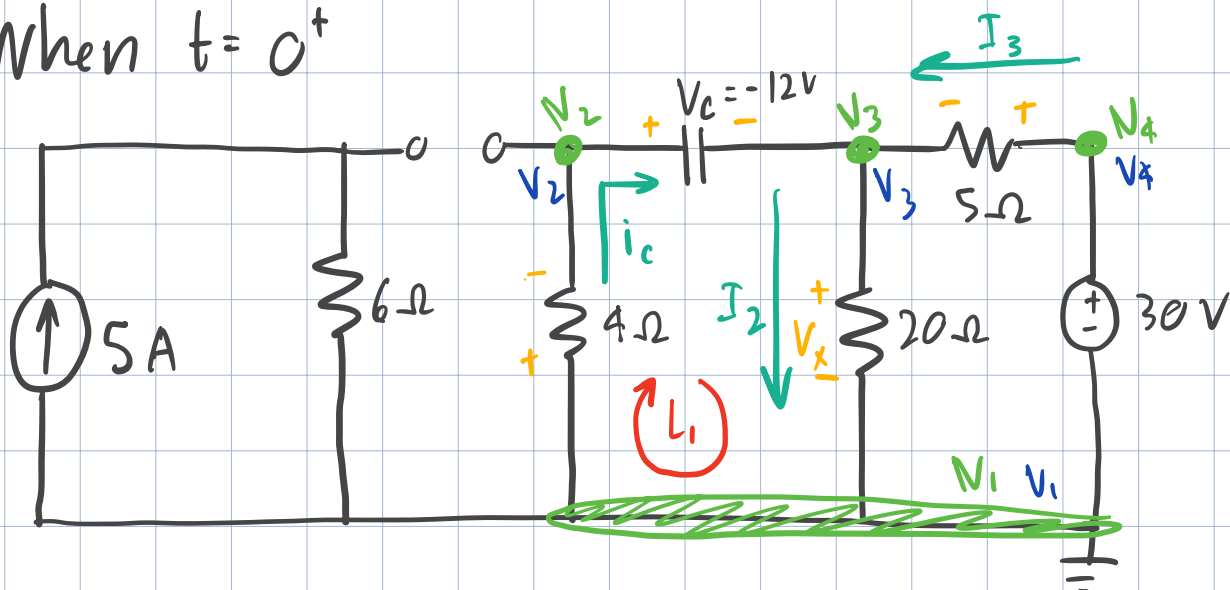

Solve for  $V_c(0^+)$

$$V_c(0^+) = V_c(0^-)$$

$$= \frac{12}{5} \cdot -5$$



$$= -12V$$

Solve for  $V_y$

Use Node Voltage Analysis

4 nodes - 1 ground - 2 voltage sources = 1 unknown

Solve for voltages

Voltages

$$\text{KCL at } V_3$$

$$I_2 = i_c + I_3$$

$$V_1 = 0V$$

$$V_4 = 30V$$

$$\frac{V_3 - V_1}{20} = \frac{V_1 - V_2}{4} + \frac{V_4 - V_3}{5}$$

$$V_3 - V_1 = 5(V_1 - V_2) + 4(V_4 - V_3)$$

$$V_3 = -5V_2 + 4V_4 - 4V_3$$

$$V_2 = V_3 - 12$$

$$V_3 = -5(V_3 - 12) + 4(30) - 4V_3$$

$$V_3 = -5V_3 + 60 + 120 - 4V_3$$

$$10V_3 = 180$$

$$V_3 = 18 \text{ V}$$

$$V_x = V_3$$

$$= 18 \text{ V}$$

Solve for  $i_c$


$$i_c = \frac{V_1 - V_2}{4}$$

$$= - \frac{V_1 - (V_3 - 12)}{4}$$

$$= - \frac{-18 + 12}{4}$$

$$= - \frac{3}{2} \text{ A}$$

When  $t = \infty$

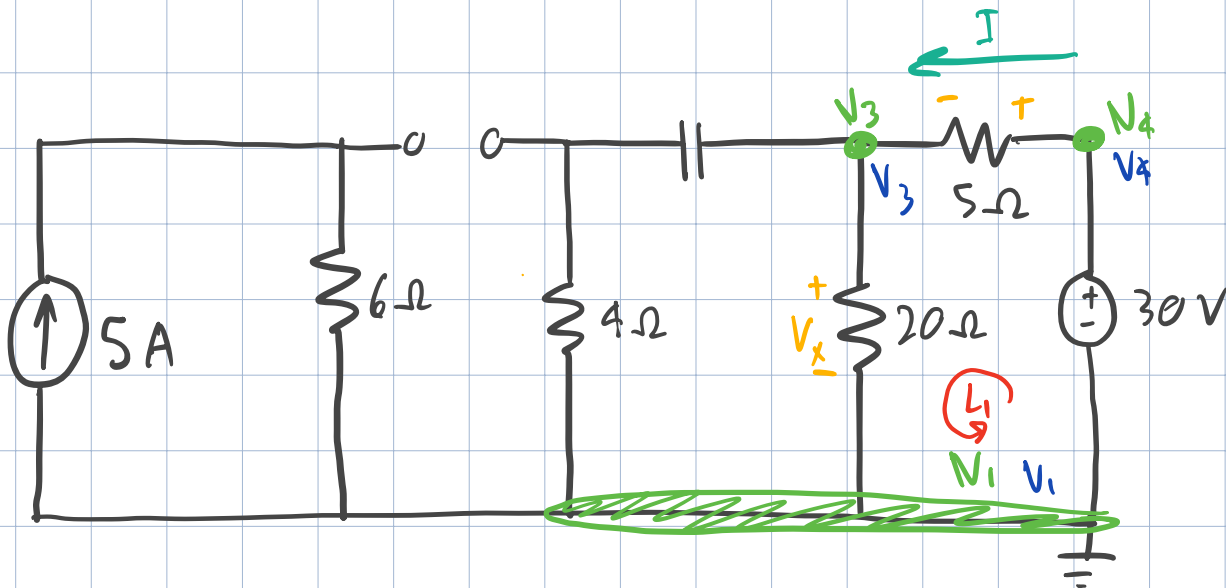

$$V_x = 24 \text{ V}$$

$$i_c = 0 \text{ A}$$

Solve for  $V_x$

$$\begin{aligned} &\text{Kvl on } L_1 \\ &30 - 5I - 20I = 0 \end{aligned}$$

$$25I = 30$$

$$I = \frac{30}{25}$$

$$= \frac{6}{5} \text{ A}$$

$$V_x = 20I$$

$$= 24 \text{ V}$$