


Homework 3

To receive full credits, you must describe the reasoning behind each step, e.g. KVL on L1, or using Ohm's law on R1, etc. Problems without reasoning receive 0 points regardless of providing correct or incorrect result. Problems with clear reasoning and correct result receives full points. Solutions with clear reasoning and incorrect results receive 3/4 of the total points.

Use the branch current method (BCM) or node voltage method (NVM) to solve the following problems. Explain why you selected such a method.


Problem 1: (10 points)

- Determine whether the diode is in the ON or OFF state. $V_\gamma = 0.7$ V.
- Solve for V_o and I_s .

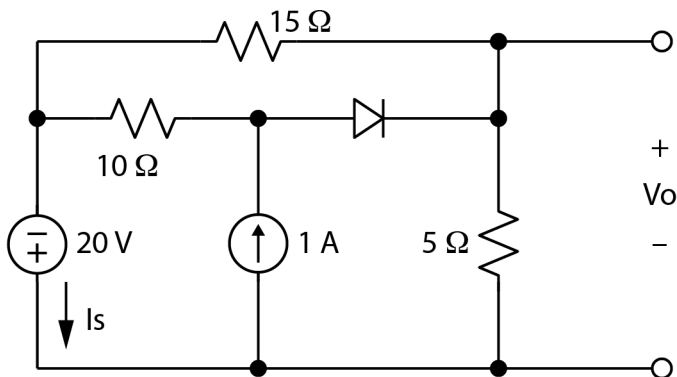


Problem 2: (10 points)

- Determine whether the diode is in the ON or OFF state. $V_\gamma = 0.7$ V.
- Solve for V_o and I_s .

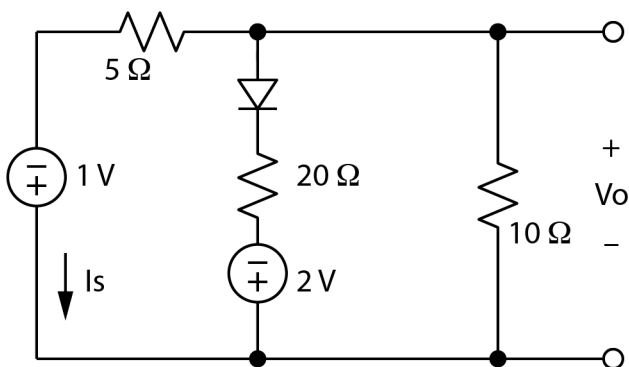


Problem 3: (20 points)

Solve for V_o . $V_\gamma = 0.7\text{ V}$.

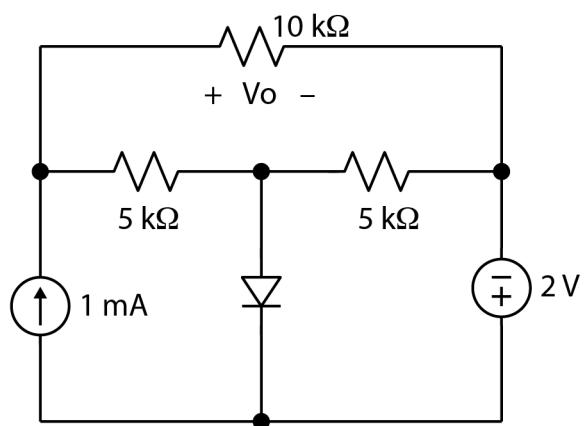


Problem 4: (30 points)

Determine the range of V_s such that the diode would be in the ON state. $V_\gamma = 0.7\text{ V}$

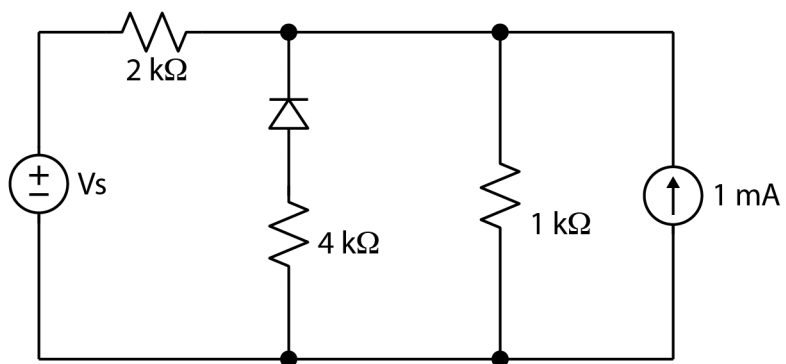


Problem 5: (20 points)

- Determine whether the diode is in the ON or OFF state. $V_\gamma = 2\text{ V}$.
- Solve for the node voltage V_x .

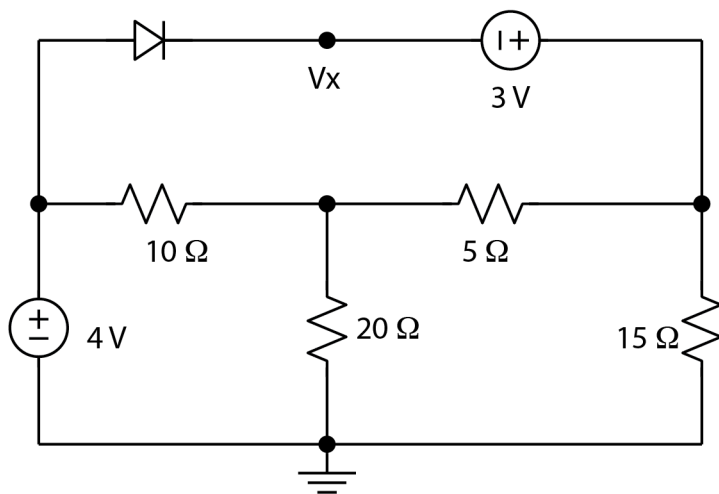

Problem 6: (10 points)

- Determine whether the diode is in the ON or OFF state. $V_\gamma = 1\text{ V}$.
- Solve for I .

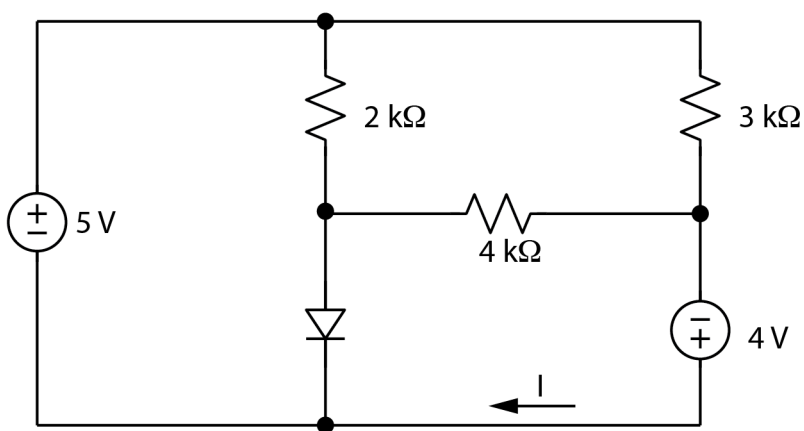

Problem 1a

4 nodes - 1 ref - 1 voltage source
= 2 unknown

Write easily found voltages

$$V_3 = 0V$$

$$V_1 + 20 = V_3 \rightarrow V_1 = -20V$$

$$V_4 = V_o$$

Kcl equations

$$\text{Kcl at } N_2: I_2 = 1$$


$$\frac{V_2 - V_1}{10} = 1$$

$$V_2 + 20 = 10$$

$$V_2 = -10V$$

$$\text{Kcl at } N_4: I_3 = I_3$$
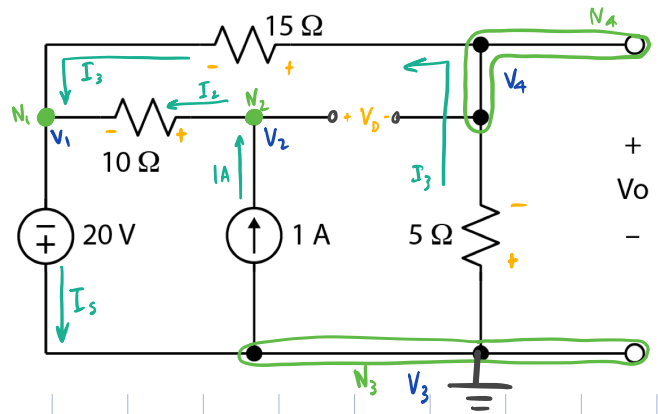
$$\frac{V_3 - V_4}{5} = \frac{V_4 - V_1}{15}$$



$$3(-V_4) = V_4 + 20$$

$$-3V_4 = V_4 + 20$$

$$-V_4 = 20$$

$$V_4 = -5$$

$$V_D = V_2 - V_4$$

$$= -10 + 5$$

$$= -5V$$

Diode is OFF

Part B

$$V_O = V_4$$

$$= -5V$$

$$\text{Kcl at } N_3: I_5 = I_2 + I_3$$

$$I_2 = 1A$$

$$I_s = 1 + I_3$$

Solve for I_3 at 5Ω resistor

$$I_3 = \frac{V_3 - V_4}{5}$$

$$= \frac{0 + 5}{5}$$


$$= 1 \text{ A}$$

$$I_s = 2 \text{ A}$$

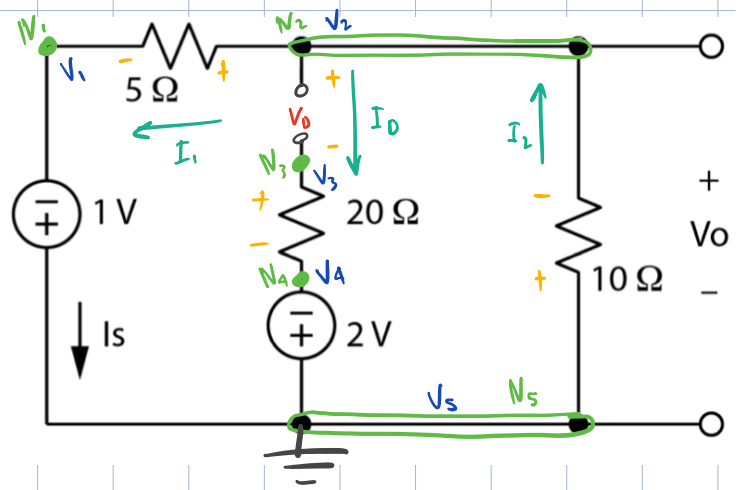Problem 2a

Start with dice in CFF

5 nodes - 1 ref - 2 voltage sources
= 2 unknown voltages



Known Voltages

$$V_5 = 0 \text{ V}$$

$I_D = 0$ A because diode is off

$$V_4 = -2V$$

$$V_1 = -1V$$

Solve for unknown voltages

KCl at N_2 : $I_1 = I_2$

$$\frac{V_2 - V_1}{5} = \frac{V_5 - V_2}{10}$$

$$\frac{V_2 + 1}{5} = \frac{-V_2}{10}$$

$$2V_2 + 2 = -V_2$$

$$3V_2 = -2$$

$$V_2 = -\frac{2}{3} \text{ V}$$

$$\text{Kcl at } N_3: 0 = \frac{V_3 - V_4}{20}$$

$$0 = V_3 + 2$$

$$V_3 = -2 \text{ V}$$

$$V_D = V_2 - V_3$$

$$= -\frac{2}{3} + 2$$

$$= \frac{4}{3} \text{ V}$$

Diode is ON


5 nodes - 1 ref - 3 voltage sources
= 1 unknown

Known Voltages

$$V_5 = 0 \text{ V}$$

$$V_4 = -2 \text{ V}$$

$$V_1 = -1 \text{ V}$$

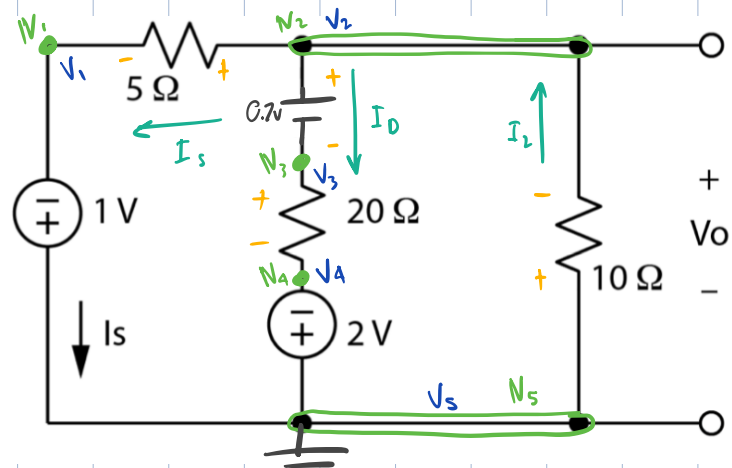

$$V_2 = V_3 + 0.7$$

Solve for I_0 at the $20\ \Omega$ resistor

$$I = \frac{V}{R}$$

$$I_0 = \frac{V_3 - V_4}{20}$$

$$\text{Kcl at } N_2: I_2 = I_s + I_0$$

$$\frac{0 - V_2}{10} = \frac{V_2 - V_1}{5} + \frac{V_3 - V_4}{20}$$

$$\frac{0 - (V_3 + 0.7)}{10} = \frac{(V_3 + 0.7) + 1}{5} + \frac{V_3 + 2}{20}$$

$$-2(V_3 + 0.7) = 4(V_3 + 1.7) + V_3 + 2$$

$$-2V_3 - 1.4 = 4V_3 + 6.8 + V_3 + 2$$

$$-7V_3 = 10.2$$

$$V_3 = -1.457\text{V}$$

$$V_2 = -0.757\text{V}$$

$$V_0 = V_2 - 0$$

$$= -0.757\text{V}$$


Solve for I_s at the 5Ω resistor

$$I_s = \frac{V_2 - V_1}{5}$$

$$= 0.0486A$$

Problem 3a

Solve with diode initially OFF

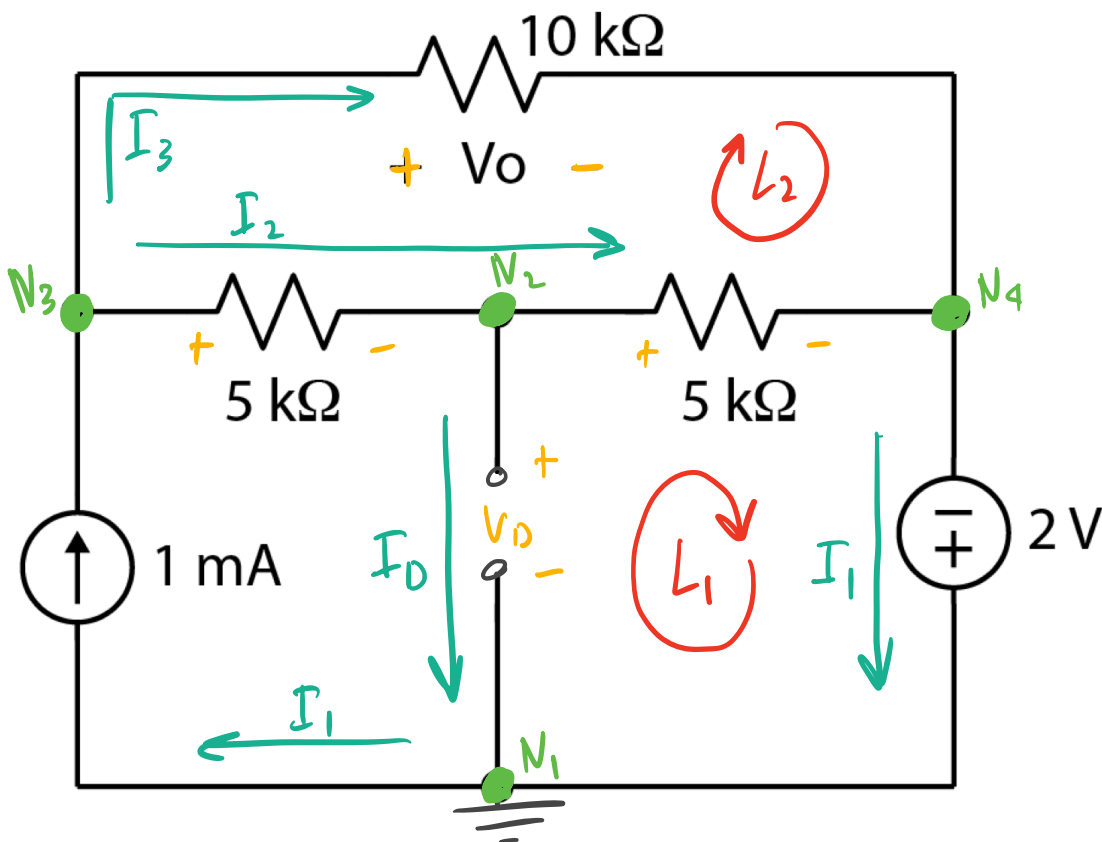

2 backyards - 1 current source = 1 unknown

4 nodes - 1 ref - 1 voltage source = 2 unknowns

Use branch current method

Known currents

$$I_D = 0$$

$$I_1 = 0.001 \text{ mA}$$

$$I_2 = 0.001 - I_3 \quad (1)$$

$$\text{Kvl on } L_2: 5000 I_2 - 10,000 I_3 + 5000 I_2 = 0$$

$$10,000 I_2 - 10,000 I_3 = 0$$

$$I_2 - I_3 = 0$$

$$I_2 = I_3 \quad (2)$$

Sub (2) into (1)

$$I_2 = 0.001 - I_2$$

$$2I_2 = 0.001$$

$$I_2 = 0.0005 \text{ A}$$

$$I_3 = 0.0005 \text{ A}$$

$$\text{Kvl on } L_1: V_0 - 5000 I_2 + 2 = 0$$

$$V_0 = 5000 I_2 - 2$$

$$= 0.5 \text{ V}$$

Diode is OFF


Solve for V_o

$$V_o = 10,000 I_3$$

$$= 5 \text{ V}$$

Problem 4a

Start with Diode OFF

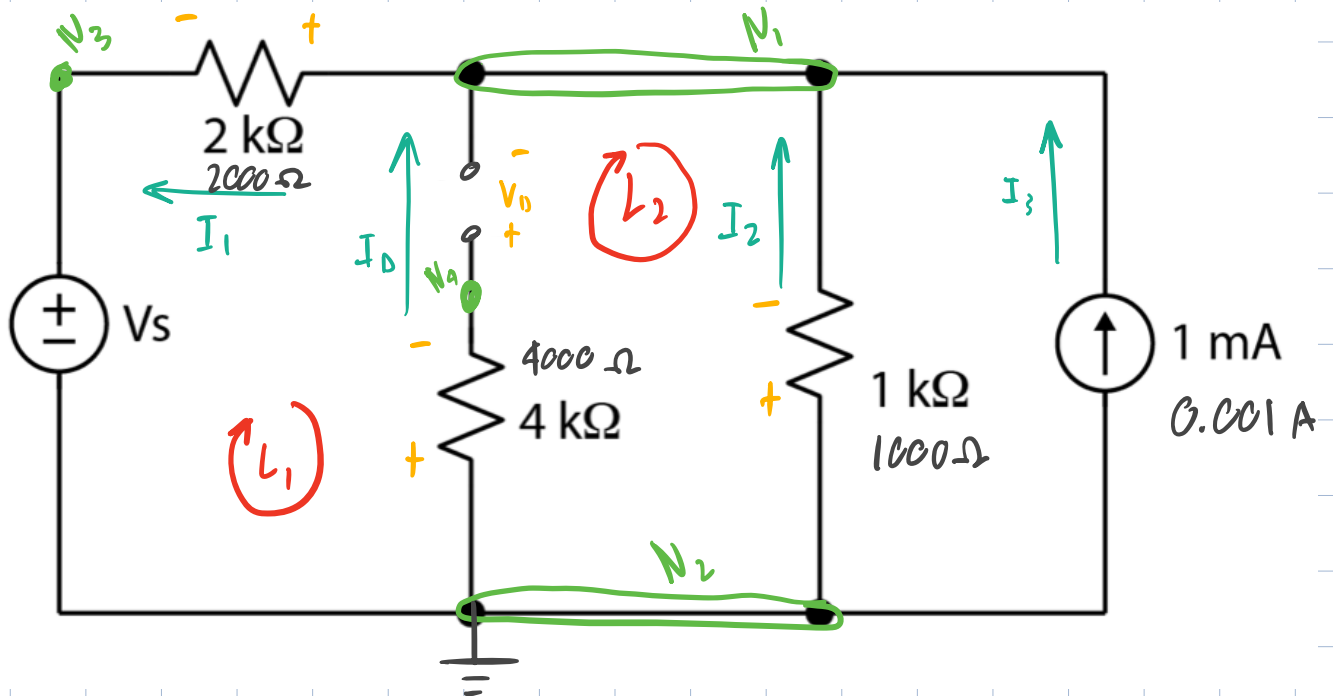

4 nodes - ref - 1 voltage source = 2 unknown

2 backwards - 1 current source = 1 unknown

Known Currents

$$I_3 = 0.001 \text{ A}$$

$$I_0 = 0 \text{ A}$$

$$I_1 = I_2 + I_3$$

$$= I_2 + 0.001$$

$$\text{Kvl on } L_1: V_s + 2000 I_1 + V_D + 4000 I_D = 0$$

$$V_s + 2000(I_2 + 0.001) + V_D = 0 \quad (1)$$

$$\text{Kvl on } L_2: 1000 I_2 - 4000 I_D - V_D = 0$$

$$1000 I_2 = 4000 I_D + V_D$$

$$I_2 = \cancel{4 I_D} + \frac{V_D}{1000}$$

$$= \frac{V_D}{1000}$$

(2)

Sub (2) into (1)

$$V_s + 2000 \left(\frac{V_D}{1000} + 0.001 \right) + V_D = 0$$

$$V_s + 2V_D + 2 + V_D = 0$$

$$-3V_D = V_s + 2$$

$$V_D = \frac{V_s + 2}{-3}$$

For the diode to be on $V_D \geq V_Y$

$$V_Y \leq \frac{V_s + 2}{-3}$$


$$-3V_Y \geq V_s + 2$$

$$V_s \leq -3V_y - 2$$


$$V_s \leq -4.1\text{V}$$

Problem 5a

Diode is ON because V is at 4 volts

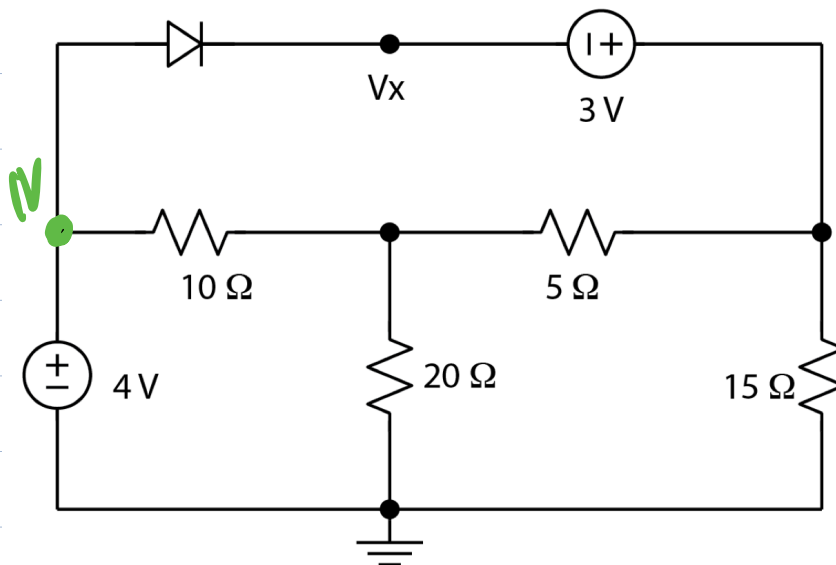

Problem 5b

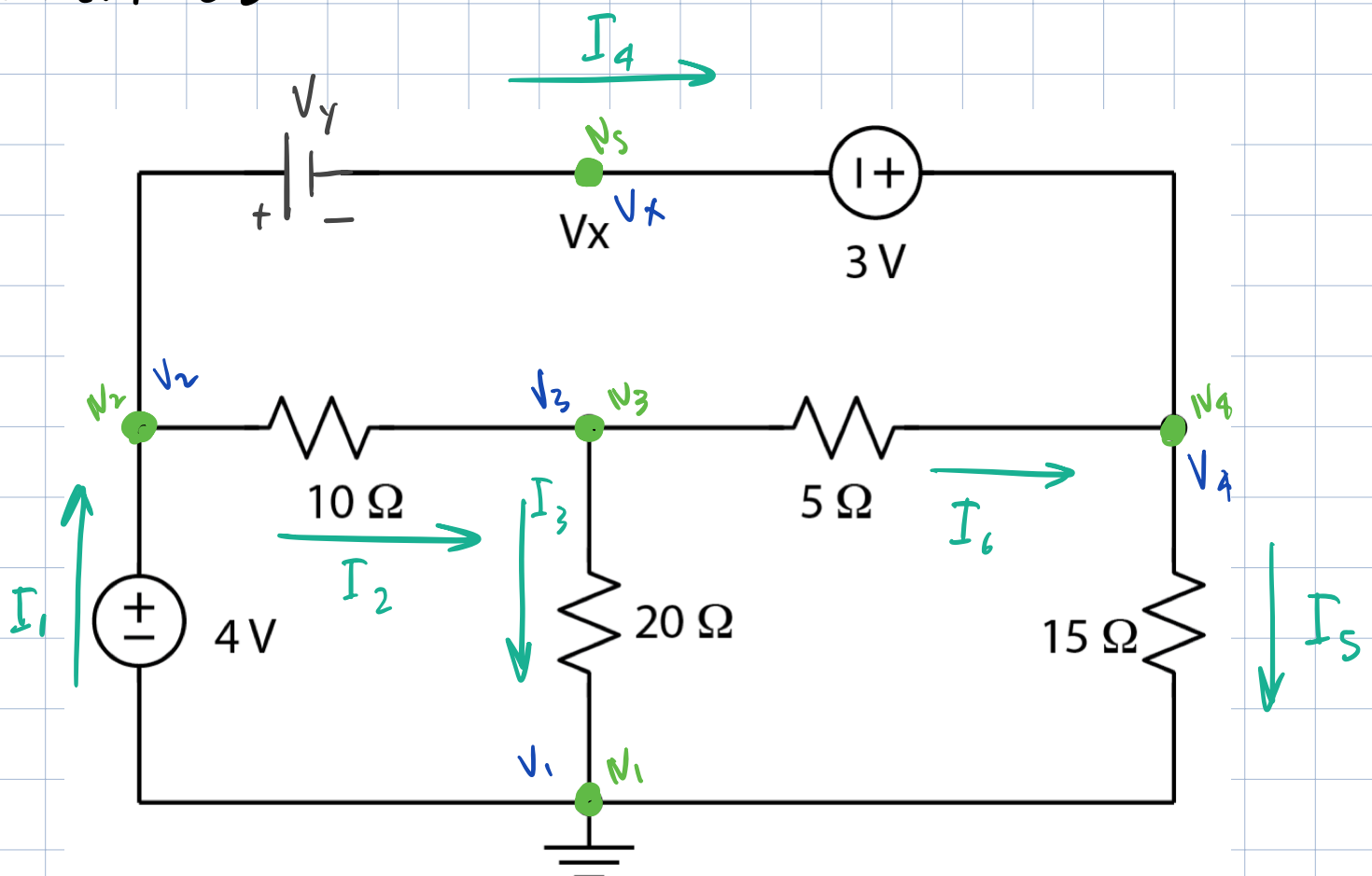

5 nodes - 1 ref - 3 voltage sources = 1 unknown

3 backwards - 0 current sources = 3 unknowns

Use node voltage method

Known voltages


$$V_1 = 0V$$

$$V_2 = 4V$$

$$\begin{aligned} V_x &= V_2 - V_1 \\ &= 2V \end{aligned}$$

Problem 6a

Start with the diode CFF

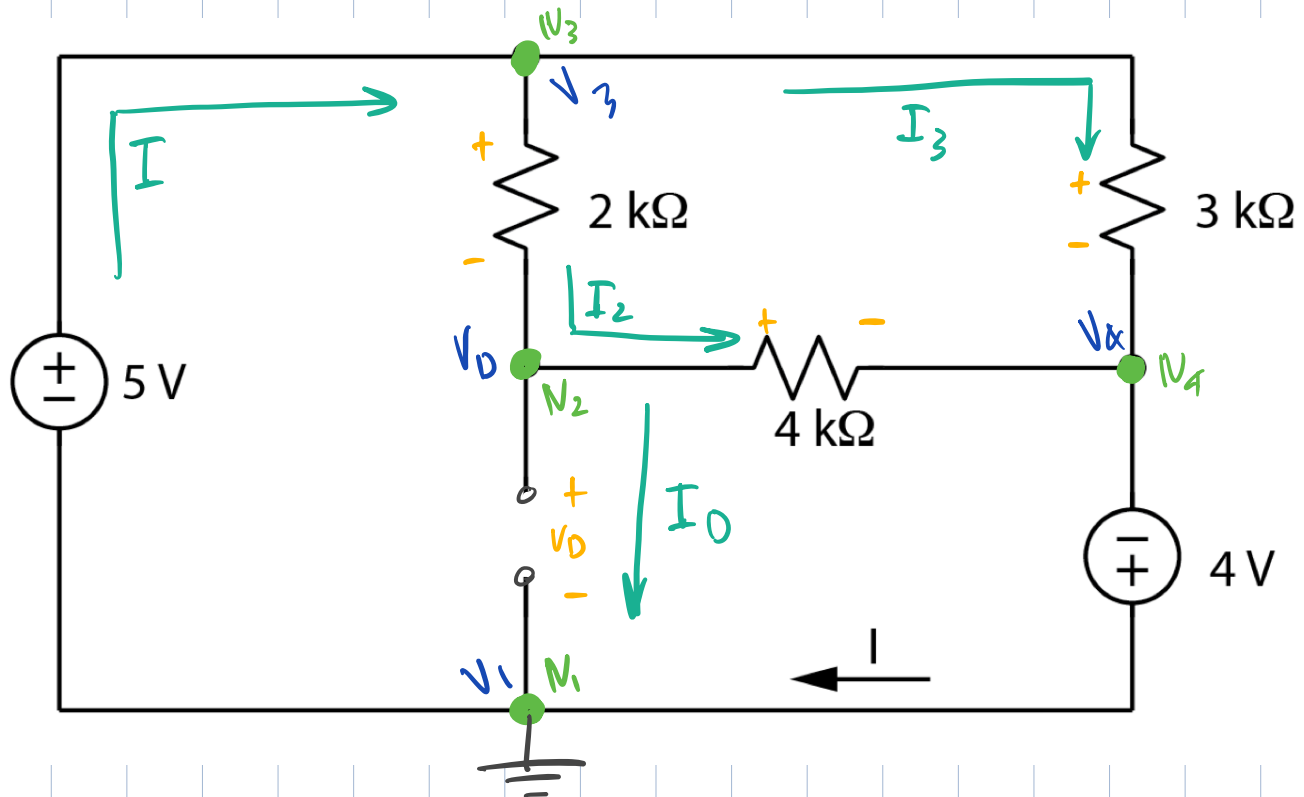

4 Nodes - 1 ref - 2 voltage sources = 1 unknown

2 branches - 0 current sources = 2 unknowns

Use node voltage analysis

Known Voltages

$$V_1 = 0V$$

$$V_3 = 5V$$

$$V_4 = -4V$$

Kcl at N_2 : $I_2 = I_2$

$$\frac{V_3 - V_0}{2000} = \frac{V_0 - V_4}{4000}$$

$$2V_3 - 2V_0 = V_0 - V_4$$


$$10 - 2V_0 = V_0 + 4$$

$$3V_0 = 6$$

$$V_0 = 2 \text{ V}$$

Diode is ON

Problem 6b

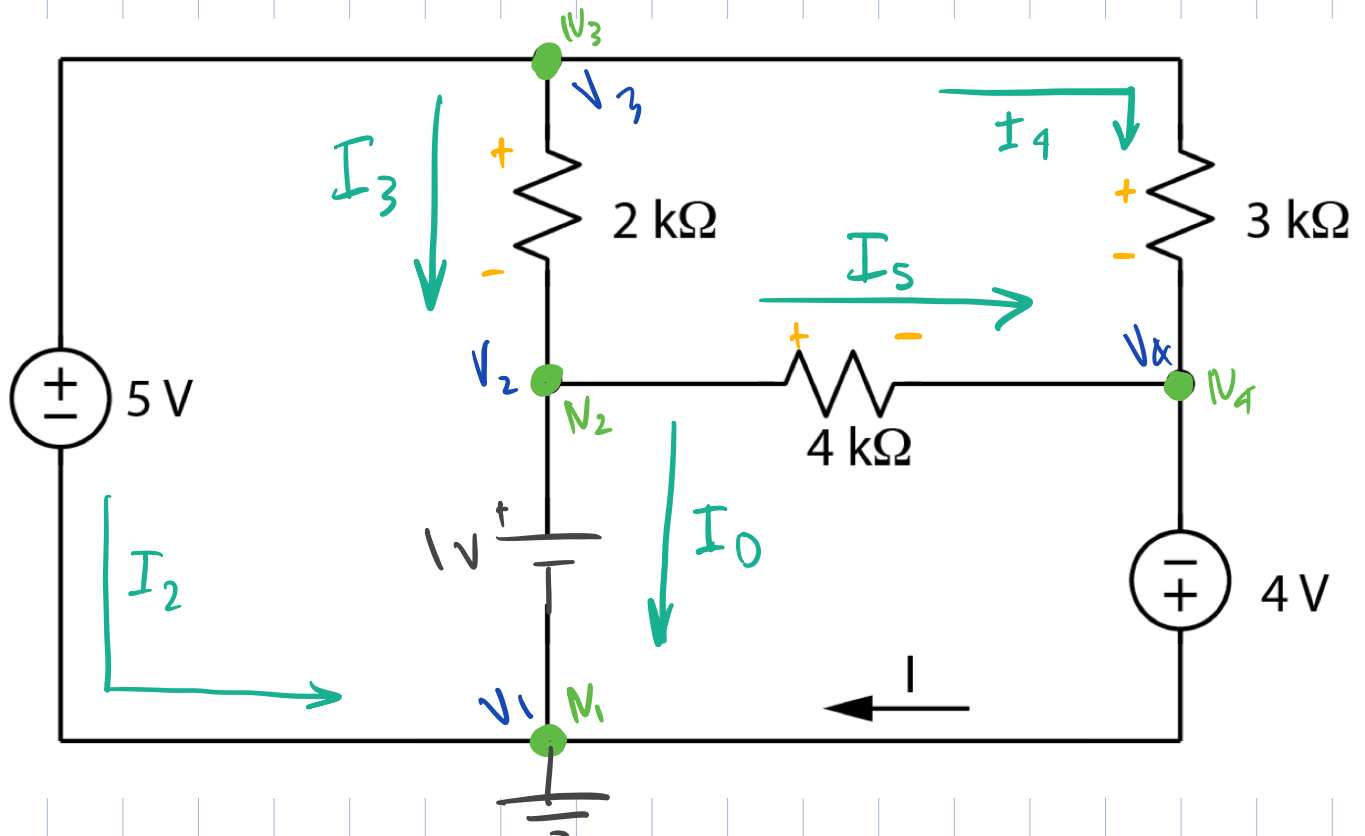

4 nodes - 1 ref - 3 voltage sources = 0 unknowns

Known voltages

$$V_1 = 0 \text{ V}$$

$$V_2 = 1 \text{ V}$$

$$V_3 = 5 \text{ V}$$

$$V_4 = -4 \text{ V}$$

Kcl at N_4 : $I_4 + I_5 = I$

$$\frac{V_3 - V_4}{3000} + \frac{V_2 - V_4}{4000} = I$$

$$I = \frac{5 + 4}{3000} + \frac{1 + 4}{4000}$$

$$= 0.00425 \text{ A}$$